

1. AB.

$$\text{ii } v_0 = (v_+ - v_-) \cdot A \quad v_- = B \cdot v_0$$

$$v_0 = (v_+ - B \cdot v_0) \cdot A$$

$$v_0 + v_0 \cdot AB = v_+ \cdot A$$

$$v_0 = \frac{A \cdot v_+}{1 + AB}$$

$$\Rightarrow v_+ = v_i \quad \text{das } \frac{A}{1 + AB}$$

2 Blok oscillator. \Rightarrow soort Schmitt-trigger.


$v_+ \neq v_- \Rightarrow$ positieve feedback.

De ~~voor~~ v_0 varieert tussen $|v_0|$ en $-|v_0|$ (of v_+ of v_-),
(voedingsspanning van opamp).

Stel $v_0 = +|v_0|$ dan zal v_- stijgen tot
 $v_- = v_0 \cdot \frac{R_2}{R_1 + R_2}$. Wanneer $v_+ = v_-$ klappt v_0 om en
 v_+ wordt $-|v_0| \cdot \frac{R_2}{R_1 + R_2}$.

Op $t=0$ zal v_0 omklappen van $-|v_0|$ naar $+|v_0|$
 dan is $v_- = -|v_0| \cdot \frac{R_2}{R_1 + R_2}$.

Deze zal stijgen tot $+|v_0|$ maar zal nooit
 'aankomen'.

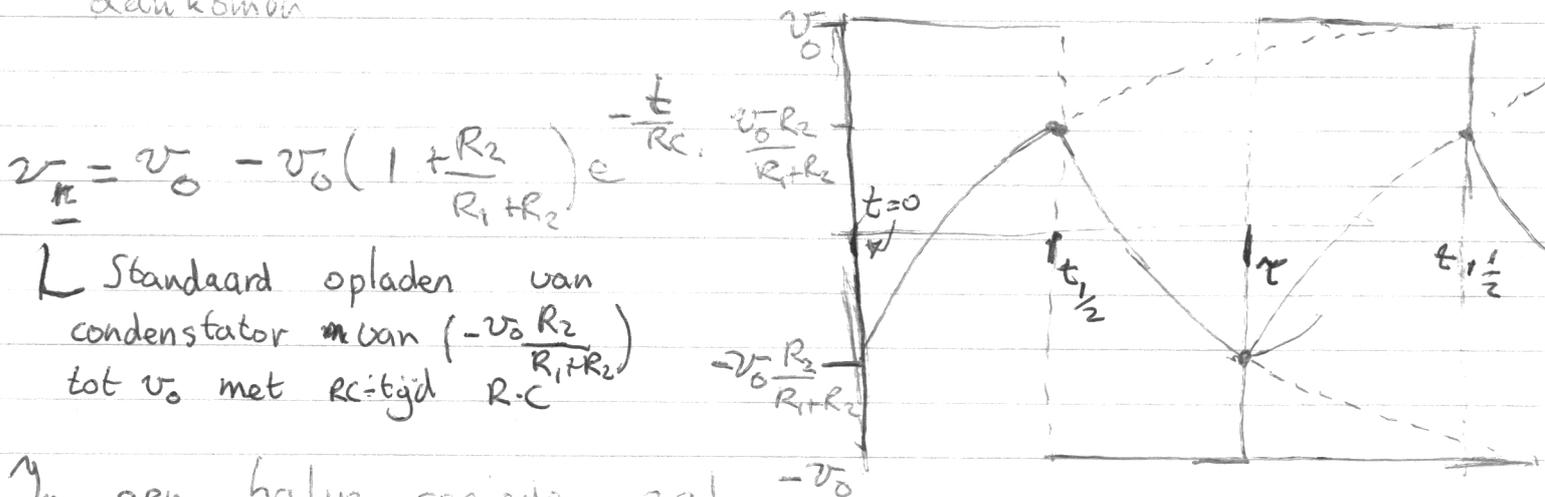

$$v_- = v_0 - v_0 \left(1 + \frac{R_2}{R_1 + R_2}\right) e^{-\frac{t}{RC} \frac{v_0 R_2}{R_1 + R_2}}$$

↳ standaard opladen van
 condensator ~~na~~ van $(-v_0 \frac{R_2}{R_1 + R_2})$
 tot v_0 met RC-tijd $R \cdot C$

In een halve periode zal
 v_- stijgen van $-v_0 \frac{R_2}{R_1 + R_2}$ ($t=0$) naar $v_0 \frac{R_2}{R_1 + R_2}$

$$v_0 \frac{R_2}{R_1 + R_2} = v_0 - v_0 \left(1 + \frac{R_2}{R_1 + R_2}\right) e^{-\frac{t}{RC}}$$

$$\left(\frac{R_2}{R_1 + R_2} - 1\right) = -\left(1 + \frac{R_2}{R_1 + R_2}\right) \cdot e^{-\frac{t}{RC}}$$

$$\frac{-R_1}{R_1 + R_2} = -\frac{R_1 + 2 \cdot R_2}{R_1 + R_2} \cdot e^{-\frac{t}{RC}} \Rightarrow e^{-\frac{t}{RC}} = \frac{+1}{1 + 2 \frac{R_2}{R_1}}$$

$$\frac{-t_{1/2}}{RC} = \ln\left(\frac{1}{1 + 2 \frac{R_2}{R_1}}\right)$$

$$t_{1/2} = RC \ln\left(1 + 2 \frac{R_2}{R_1}\right)$$

$$T = 2 t_{1/2} = 2RC \ln\left(1 + 2 \frac{R_2}{R_1}\right) \quad f = \frac{1}{T}$$

	code	Q ₃	Q ₂	Q ₁	J ₃ k ₃	J ₂ k ₂	J ₁ k ₁
3	1	0	0	1	0 X	1 X	X 0
	3	0	1	1	1 X	X 1	X 0
	5	1	0	1	X 0	1 X	X 0
	7	1	1	1	X 0	X 0	X 1
	6	1	1	0	X 0	X 1	0 X
	4	1	0	0	X 1	1 X	0 X
	2	0	1	0	0 X	X 1	1 X
	1	0	0	1			

$J_2 = 0$

J k	Q	Q	J k
0 0	gelyk.	0	1 X
0 1	0	1	X 0
1 0	1	0	X 1
1 1	toegke.	0	0 X

K ₁	Q ₃	Q ₂	Q ₁	
	0	X	0	0 X
	1	X	0	1 X
			1	1 X
			0	0 X

$\Rightarrow k_1 = Q_2 \cdot Q_3$

J ₁	Q ₃	Q ₂	Q ₁	
	0	X	X	X 1
	1	0	X	X 0

$\Rightarrow J_1 = Q_2 \cdot Q_3$

K ₂	Q ₃	Q ₂	Q ₁	
	0	X	X	1 1
	1	X	X	0 1


$\Rightarrow k_2 = Q_1 \cdot Q_3$

J ₂ = 1	Q ₃	Q ₂	Q ₁	
	0	X	X	X X
	1	1	0	0 0

$\Rightarrow k_3 = Q_1 + Q_2 = \overline{Q_1} \cdot \overline{Q_2}$

J ₃	Q ₃	Q ₂	Q ₁	
	0	X	0	1 0
	1	X	X	X X

$\Rightarrow J_3 = Q_1 \cdot Q_2$

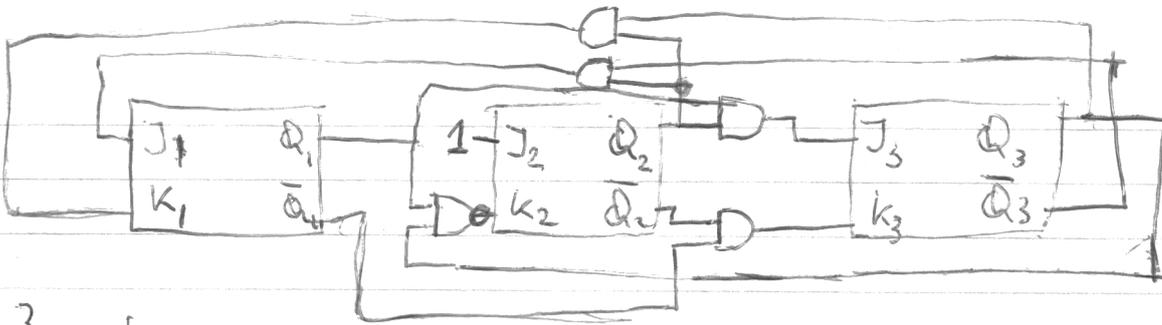


3 uervolg

1	0	0	1
3	0	1	1
5	1	0	1
7	1	1	1
6	1	1	0
4	1	0	0
2	0	1	0
1	0	0	1

~~xxx~~



4

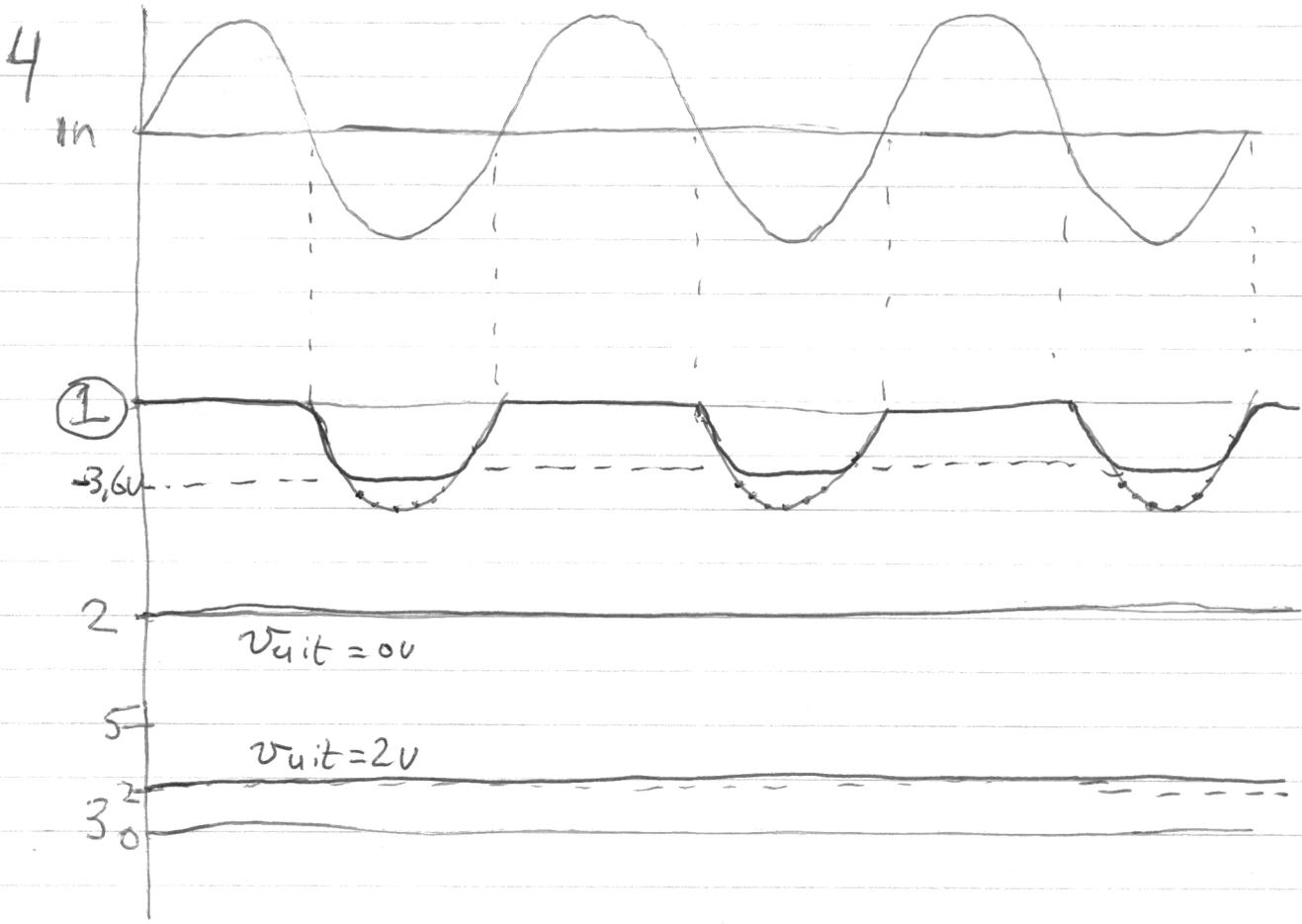Dat kan niet: Q_2 is degene die het vaakst als klok kan werken Q_1 en Q_3 moeten echter ook schakelen wanneer Q_2 gelijk blijft.
Dat zelfde geldt als Q_1 of Q_3 als klok zouden werken




5.1

$$i_d' = g_m v_{gs}$$

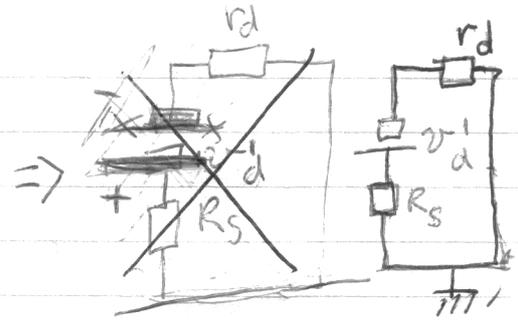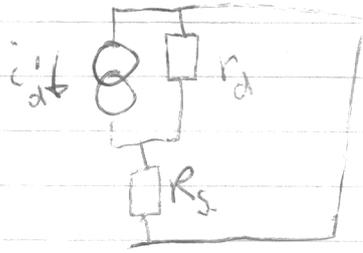

$$v_d' = i_d' r_d$$

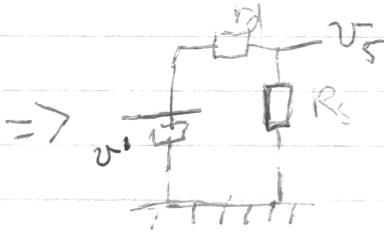

$$v_s = \frac{v_s' \cdot R_s}{R_s + r_d} = g_m v_{gs} \frac{r_d R_s}{R_s + r_d}$$

$$\Rightarrow v_s = g_m (v_g - v_s) \cdot R_s \parallel r_d$$

~~$$v_s (1 + g_m R_s \parallel r_d) = g_m v_g R_s \parallel r_d$$~~

$$v_s (1 + g_m R_s \parallel r_d) = g_m v_g R_s \parallel r_d$$

$$v_s = \frac{v_g g_m R_s \parallel r_d}{(1 + g_m R_s \parallel r_d)}$$

5.2. Als $r_d \gg R_s$ dan $r_d \parallel R_s \approx R_s$

Dus
$$v_s = \frac{v_g g_m R_s}{1 + g_m R_s}$$

En als $g_m R_s \gg 1$ dan $\frac{g_m R_s}{1 + g_m R_s} \approx 1$

Dus $v_s \approx v_g$ en $\frac{v_o}{v_i} = \frac{v_s}{v_g} \approx 1$