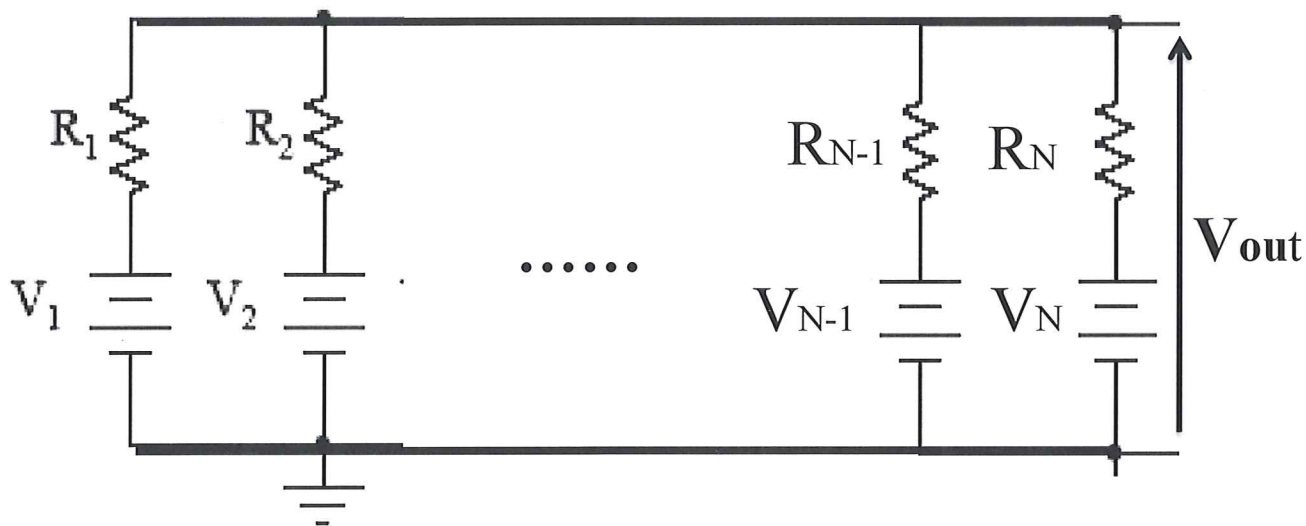


Problem 1 (2 points)


(a: 1 point)



Prove that:

$$V_{out} = \left(\sum_{i=1}^N \frac{V_i}{R_i} \right) / \left(\sum_{i=1}^N \frac{1}{R_i} \right)$$

(b: 1 point)

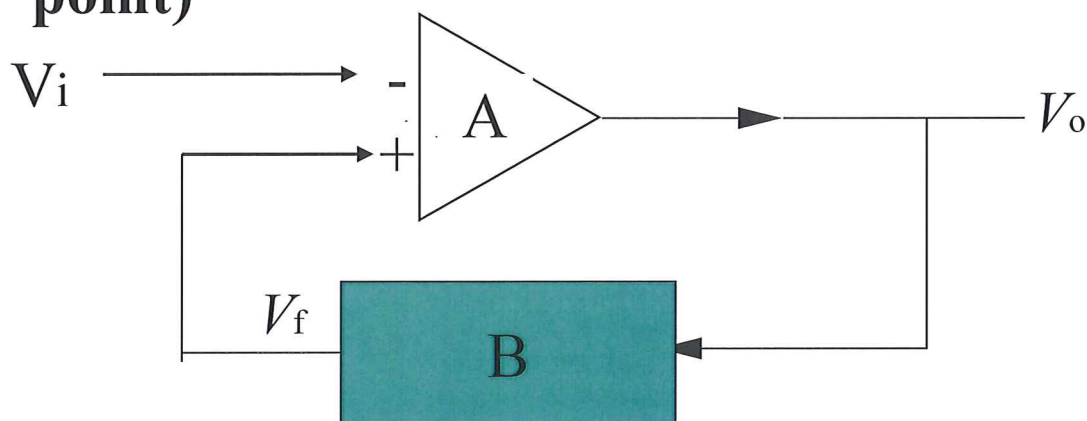


Calculate the loop gain $G=V_o/V_i$ and indicate the condition for possible oscillation

Problem 2 (2 points)


$$V_+ = V_-$$

(a: 1 point)

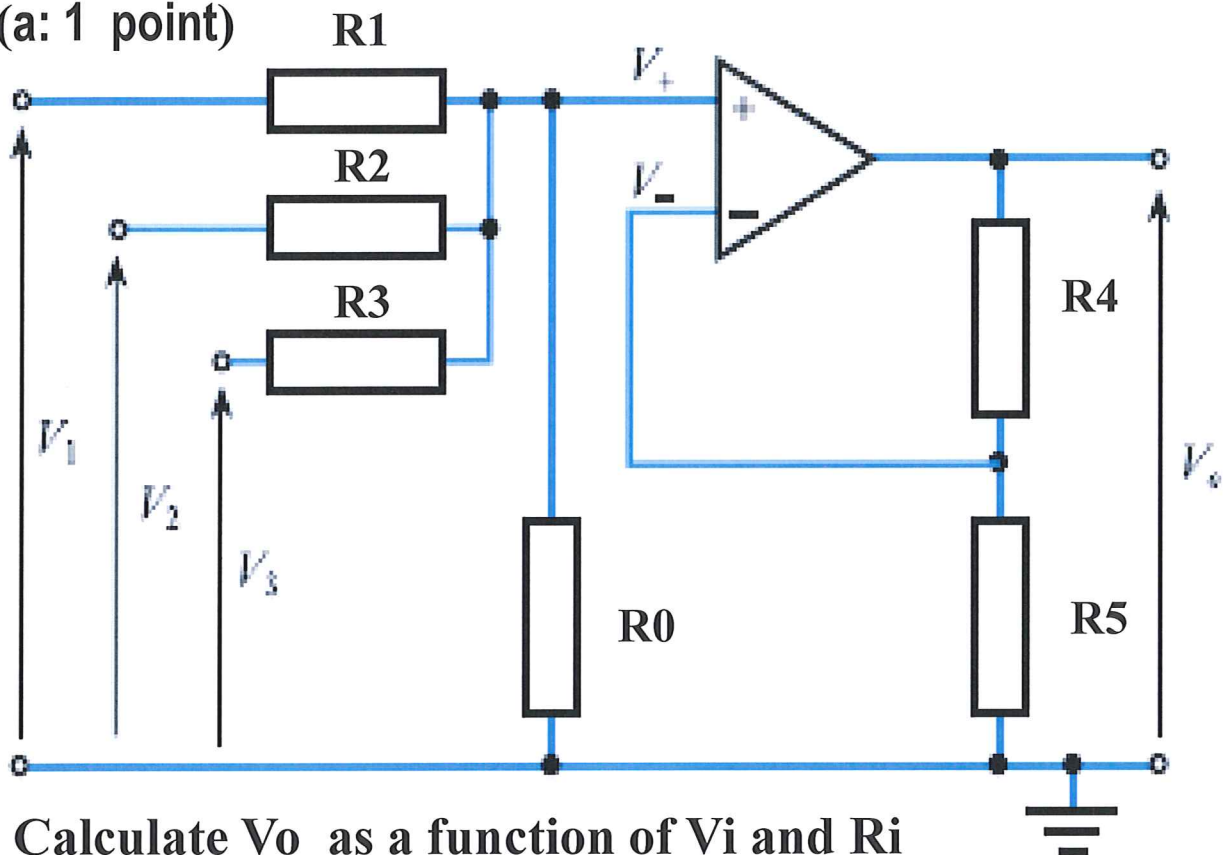

Calculate V_o as a function of V_i and R_i

(b: 1 point)

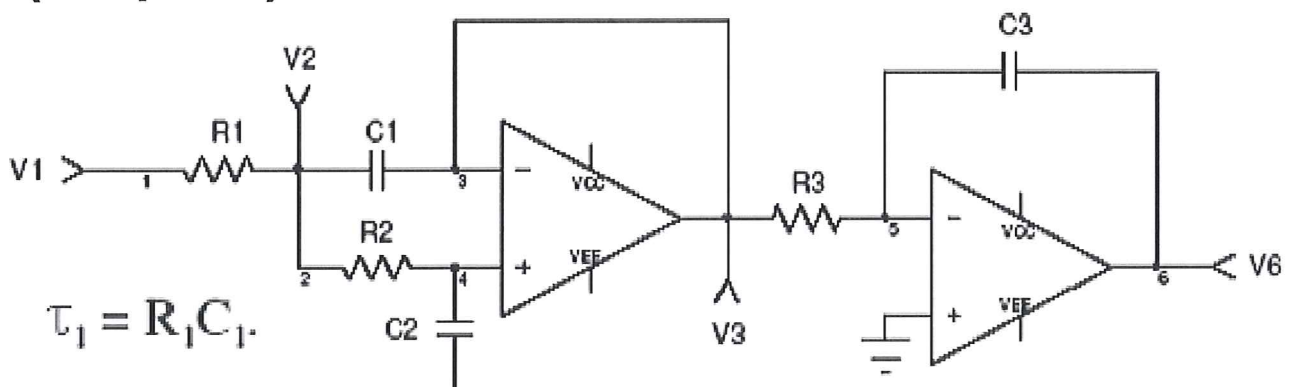


$$\tau_1 = R_1 C_1$$


Prove that:
$$v(2) = \frac{\left(\frac{R_1}{R_2} + j\omega\tau_1\right) V(3) + V(1)}{1 + \frac{R_1}{R_2} + j\omega\tau_1}$$

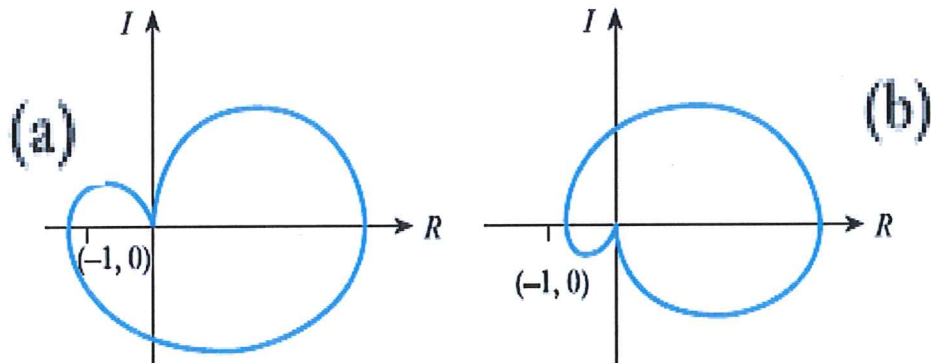Problem 3 (1.5 points)

(a: 0.5 point) -The Nyquist diagrams below represent two circuits. Determine the number of low-frequency and high-frequency cut-offs and indicate which system is stable



(b:1 point)

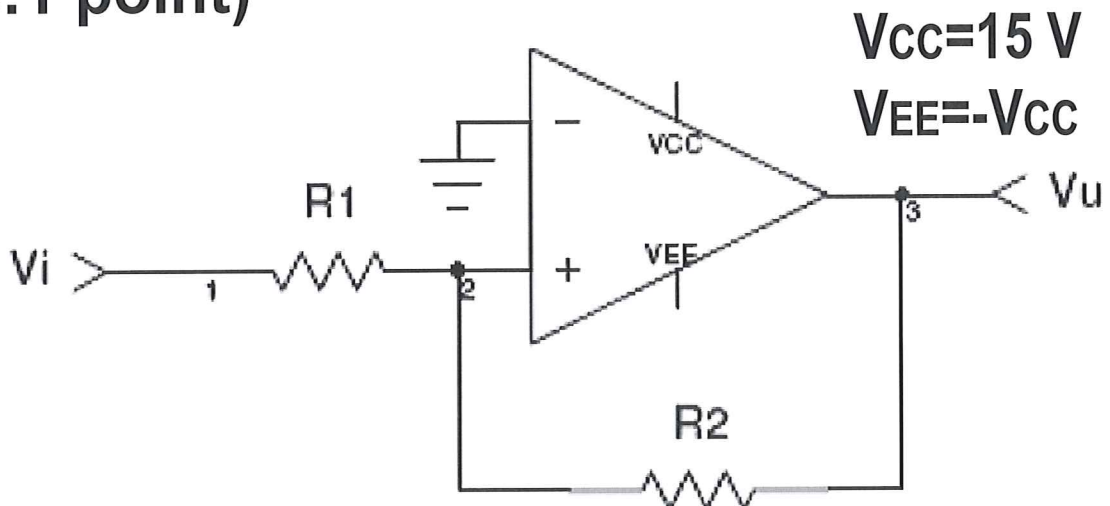

Assume that $R1=3\text{ K}\Omega$, $R2=15\text{ K}\Omega$ input potential

$V_i = V_{oi} \sin(\omega t)$, $V_{oi} = 5\text{ V}$

→ Draw the output potential V_u :

Problem 4 (2 points)

(a: 1 point)

	Before			After		
	Q3	Q2	Q1	Q3	Q2	Q1
1						
2						
3						
4						


J	K	Q_n
0	0	Q_{n-1}
0	1	0
1	0	1
1	1	$\overline{Q_{n-1}}$

Q_{n-1}	Q_n	J	K
0	0	0	*
0	1	1	*
1	0	*	1
1	1	*	0

*: don't care




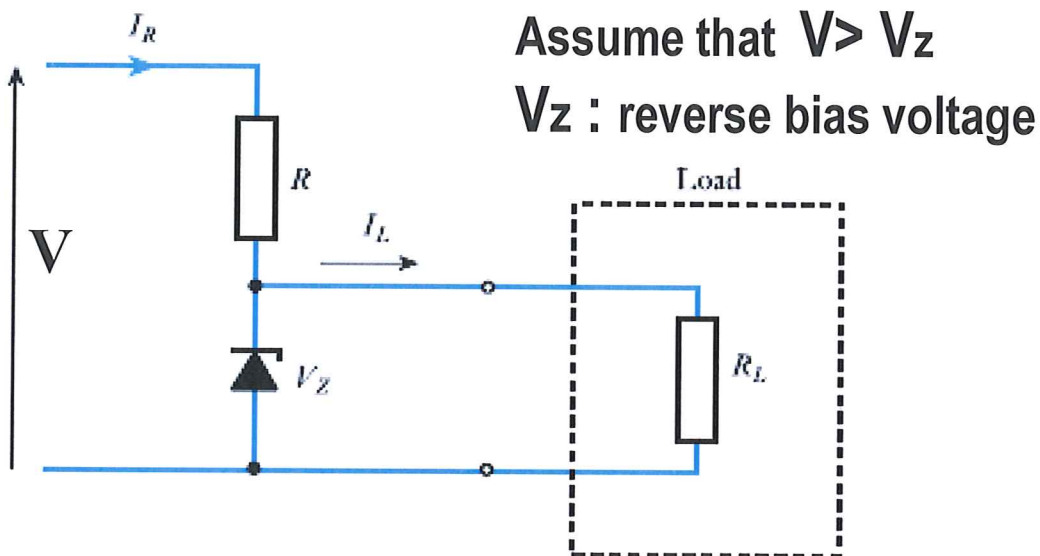



Build a synchronous 4-counter (1→4)

(b: 1 point)

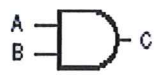

For what value of R the zener diode can not conduct current under reverse bias conditions ?

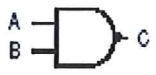
Tabel 1 Logische poorten.

Funcie	Symbol	Boolean	Waarheidstabel															
AND		$C = A \cdot B$	<table border="1"> <tr><td>A</td><td>B</td><td>C</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	A	B	C	0	0	0	0	1	0	1	0	0	1	1	1
A	B	C																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$C = A \times B$	<table border="1"> <tr><td>A</td><td>B</td><td>C</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	A	B	C	0	0	0	0	1	1	1	0	1	1	1	1
A	B	C																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
NOT		$B = \overline{A}$	<table border="1"> <tr><td>A</td><td>B</td></tr> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </table>	A	B	0	1	1	0									
A	B																	
0	1																	
1	0																	
NAND		$C = \overline{A \cdot B}$	<table border="1"> <tr><td>A</td><td>B</td><td>C</td></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> </table>	A	B	C	0	0	1	0	1	1	1	0	1			
A	B	C																
0	0	1																
0	1	1																
1	0	1																
NOR		$C = \overline{A \times B}$	<table border="1"> <tr><td>A</td><td>B</td><td>C</td></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	A	B	C	0	0	1	0	1	0	1	0	0	1	1	0
A	B	C																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
XOR		$C = A \oplus B$	<table border="1"> <tr><td>A</td><td>B</td><td>C</td></tr> <tr><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td></tr> </table>	A	B	C	0	0	0	0	1	1	1	0	1	1	1	0
A	B	C																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
XNOR		$C = \overline{A \oplus B}$	<table border="1"> <tr><td>A</td><td>B</td><td>C</td></tr> <tr><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td></tr> </table>	A	B	C	0	0	1	0	1	0	1	0	0	1	1	1
A	B	C																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

Problem 5 (2.5 points)

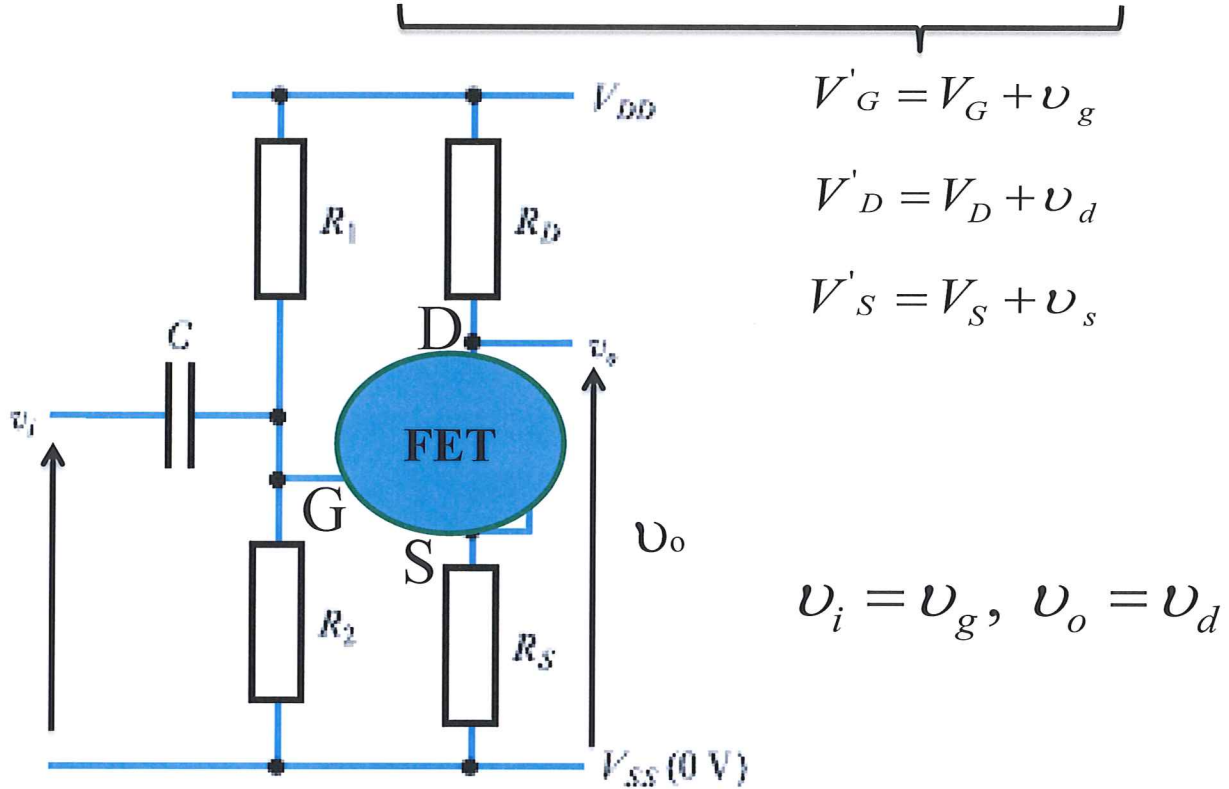(a) (1 point):

If an application of a small varying input signal v_i leads to small variation of the gate, drain, and source potentials :



Then show that the current I_D through the FET changes up to first order terms as:


$$I'_D \approx I_D + \left\{ g_m v_{gs} + \frac{v_{ds}}{r_d} \right\} + \dots$$

$$I_D = I_D(V_{GS}, V_{DS})$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}}, \quad 1/r_d = \frac{\partial I_D}{\partial V_{DS}} \quad v_{gs} = v_g - v_s, \quad v_{ds} = v_d - v_s$$

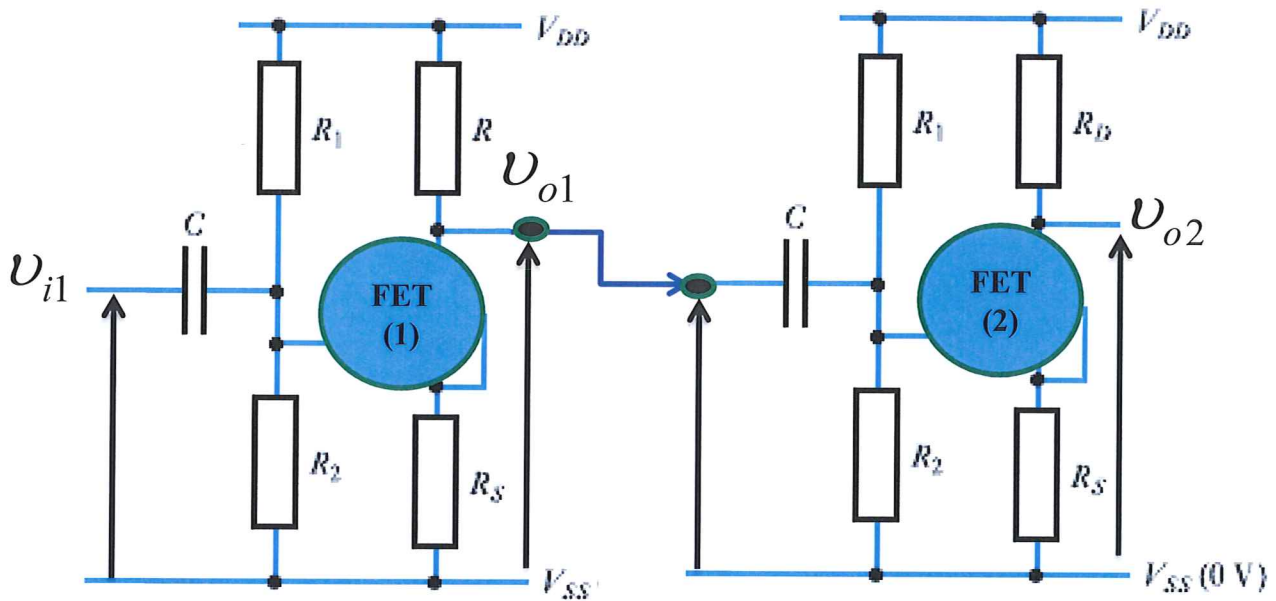(b) FET amplifier (1.5 points)

Consider a cascade of two FETs in series where the output of FET(1) is the input at the gate for FET (2) :



Show that the total amplification ratio is given by (1 point):

$$\frac{v_{o2}}{v_{i1}} = \left\{ \frac{g_m R_D}{1 + g_m R_S + [(R_D + R_S) / r_d]} \right\}^2$$

For $R_{D,S} \ll r_d$, and $g_m R_S \gg 1$ derive

a simpler expression for v_{o2}/v_{i1} (0.5 points)

Tip: For (b) use the knowledge from (a) or make directly the “small signal circuits of the FETs in series to compute the amplification ratio ”