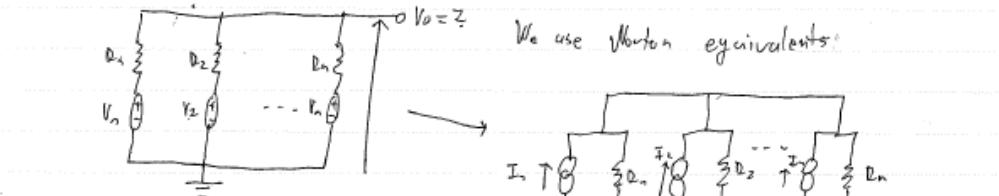


# Exam-solution-finalApril-2014


## Problem-1

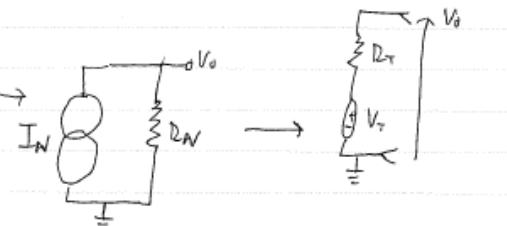Problem 1a:



$$I_{\text{N}} = \frac{V_0}{R_n}$$

resistors are parallel, current sources also




$$I_{\text{N}} = \sum_i I_i = \sum_i \frac{V_i}{R_i}$$

$$R_N = \frac{1}{\sum_i \frac{1}{R_i}} = R_T$$

$$V_0 = I_{\text{N}} R_N = \frac{\sum_i V_i}{\sum_i \frac{1}{R_i}}$$

Problem 2a):

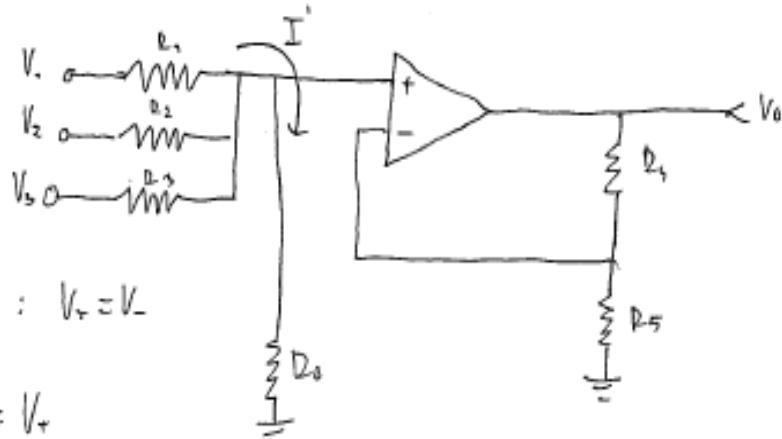

negative feedback:  $V_r = V_-$

$$V_- = V_0 \frac{R_5}{R_5 + R_4} = V_r$$

$$I^+ = \frac{V_r - V_+}{R_2} + \frac{V_2 - V_r}{R_3} + \frac{V_3 - V_r}{R_4} = \frac{V_+}{R_0} = \frac{V_1}{R_1} - \frac{V_r}{R_1} + \frac{V_2}{R_2} - \frac{V_r}{R_2} + \frac{V_3}{R_3} - \frac{V_r}{R_3} \rightarrow V_r \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_0} \right) = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$


$$V_0 \frac{R_5}{R_5 + R_4} \cdot \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{V_1}{R_1}$$

$$V_0 = \left( 1 + \frac{R_4}{R_5} \right) \frac{\sum \frac{V_i}{R_i}}{\frac{1}{R_1} + \sum \frac{1}{R_i}}$$

$$\text{or explicitly } V_0 = \left( 1 + \frac{R_4}{R_5} \right) \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_0}}$$

↑ probably very big

Problem 1b) :

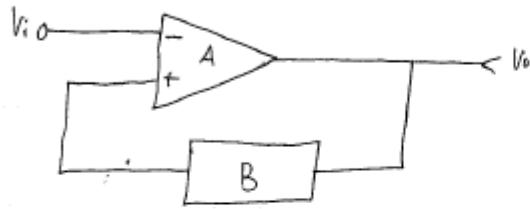


$$\rightarrow \text{positive feedback} : V_o = A(V_t - V_i) \quad ; \quad V_t = BV_o, \quad V = V_i$$

$$V_o = ABV_o - AV_i \quad \rightarrow \quad V_o(1 - AB) = -AV_i$$



$$\rightarrow G = \frac{V_o}{V_i} = \frac{AV_i - A}{1 - AB} \quad \xrightarrow{\underline{\underline{1 - AB}}} \quad \begin{aligned} &\rightarrow \text{oscillations when } AB = 1 \\ &\rightarrow \left. \begin{aligned} \operatorname{Re}(AB) &= 1 \\ \operatorname{Im}(AB) &= 0 \end{aligned} \right\} \varphi = 0^\circ, \quad AB = 0 \text{ dB} \end{aligned}$$

Problem 2b)

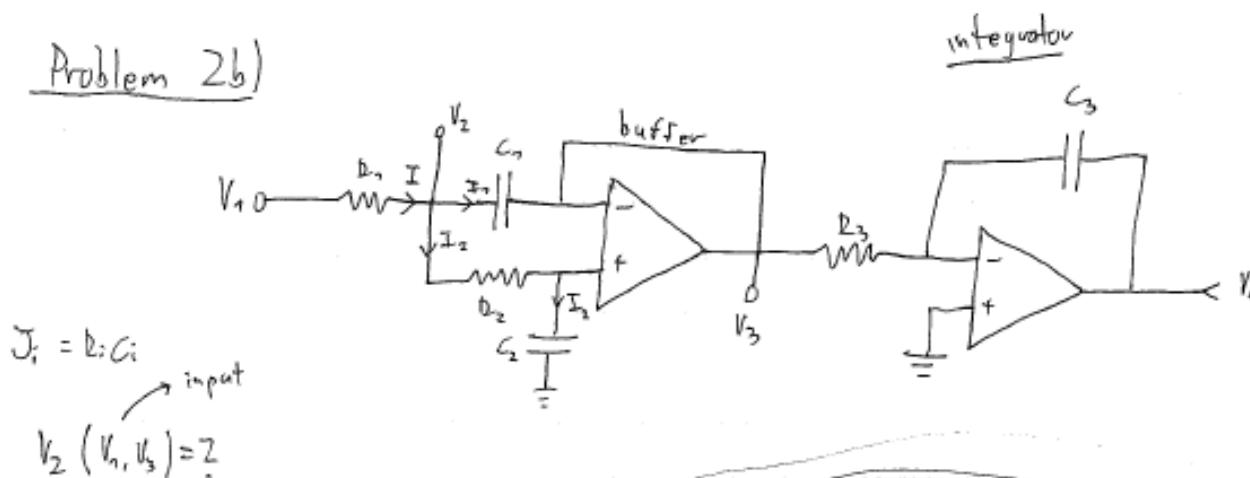

$$J_i = D_1 C_1$$

*input*

$$V_2(V_1, V_3) = ?$$



$$V_3 = V_4 \rightarrow I = I_1 + I_2 \rightarrow \frac{V_1 - V_2}{D_1} = \frac{V_2 - V_3}{Z_{C_1}} + \frac{V_2 - V_3}{D_2} = (V_2 - V_3) \left( i\omega D_1 C_1 + \frac{1}{D_2} \right)$$

$$V_1 - V_2 = (V_2 - V_3) \left( i\omega D_1 C_1 + \frac{1}{D_2} \right)$$

$$V_2 \left( 1 + \frac{D_1}{D_2} + i\omega J_1 \right) = V_1 + V_3 \left( \frac{D_1}{D_2} + i\omega J_1 \right)$$

$$\boxed{V_2 = \frac{V_1 + V_3 \left( \frac{D_1}{D_2} + i\omega J_1 \right)}{1 + \frac{D_1}{D_2} + i\omega J_1}}$$

Problem 3a)

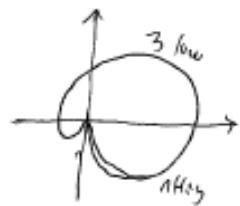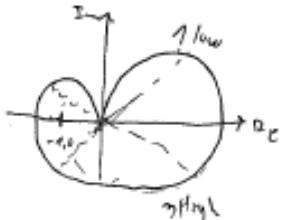

System (a) has:

- 1 low cut-off
- 3 high cut-offs
- very unstable (possible oscillations)
  - ↳ at high frequencies

System (b) has :

- 3 low
- 1 high
  - ↳ positive feedback
- unstable at low frequencies, but no oscillations


Problem 3b) Schmitt trigger

$$V_{ce} = 15V$$

$$V_{ce} = -15V$$

$$\begin{aligned} R_1 &= 3k \quad \left\{ \frac{R_1}{R_2} = \frac{1}{5} = 0.2 \right. \\ R_2 &= 75k \end{aligned}$$

$$V_i = 5V \cdot \sin(\omega t)$$

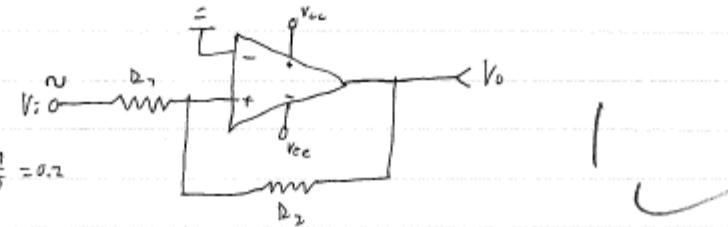

$$\frac{V_f - V_+}{R_1} = \frac{V_+ - V_0}{R_2} \rightarrow \frac{V_+ + V_0}{R_2} = \frac{V_i + V_0}{R_1}$$


$$V_+ \frac{R_1 + R_2}{R_1 R_2} = \frac{V_i R_2 + V_0 R_1}{R_1 R_2}$$

$$V_+ = V_i \frac{R_2}{R_1 + R_2} + V_0 \frac{R_1}{R_1 + R_2}$$

$$V_0 = \pm 75V \rightarrow \text{it switches when } V_+ = 0$$

$$\rightarrow V_i = -V_0 \frac{R_1}{R_2} = \pm 3V$$

$$V_0 = V_i \cdot \frac{25}{75} + 10 \frac{3}{75} = \frac{V_i 5}{6} + V_0 \frac{2}{6} = \frac{5}{6} V_i \pm 2.5V$$

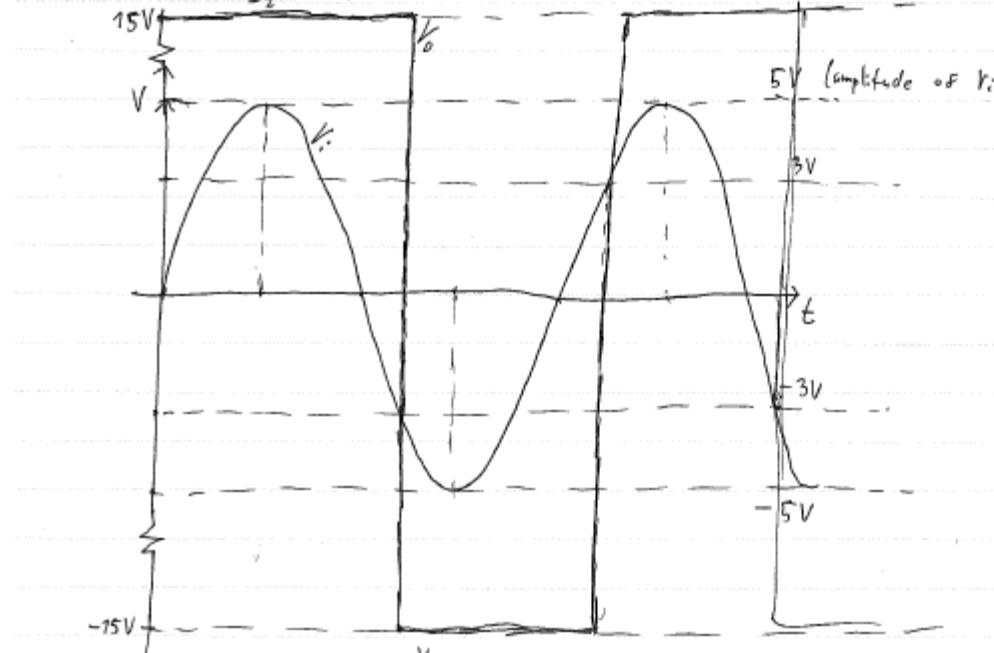

Problem 6a)

7 → 4 counter

	$Q_3\ Q_2\ Q_1$	$Q_3\ Q_2\ Q_1$	$J_3\ K_3$	$J_2\ D_2$	$J_1\ D_1$
1	0 0 1	0 1 0	0 x	1 x	x 1
2	0 1 0	0 1 1	0 x	x 0	1 x
3	0 1 1	1 0 0	1 x	x 1	x 1
4	1 0 0	0 0 1	x 1	0 x	1 x

$J_3 = D_2 = 1$

$J_3$

$Q_3$	00	01	11	10
0	X	0	1	0
1	X	X	X	X

$D_3$

$Q_3$	00	01	11	10
0	X	X	X	X
1	X	X	X	X

$J_2$

$Q_2$	00	01	11	10
0	X	1	X	X
1	0	X	X	X




$D_2$

$Q_2$	00	01	11	10
0	X	1	X	0
1	X	X	X	X


$$J_3 = Q_2 Q_1, \quad D_3 = 1$$

$$J_2 = Q_1, \quad D_2 = Q_1 = J_2$$

/ could also put  $J_2 = \bar{Q}_3$

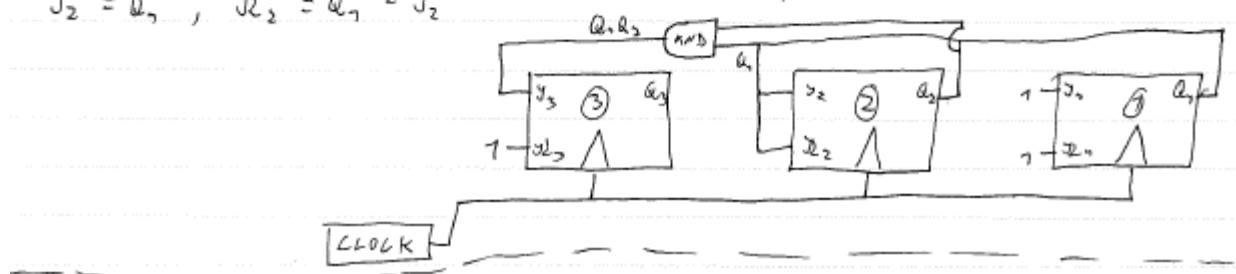

Problem 4b)

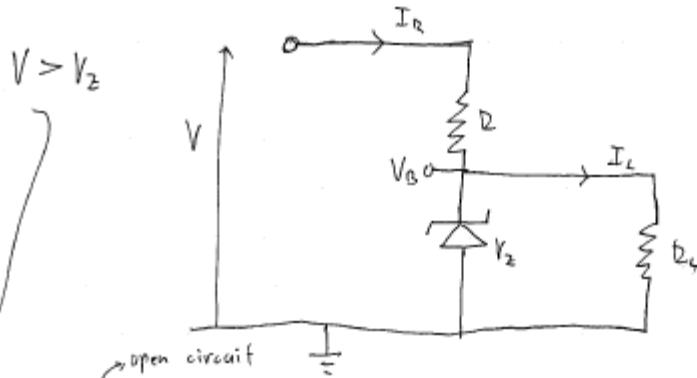

When Zener doesn't conduct:  $I_R = I_L$        $\frac{V - V_B}{R} = \frac{V_B - 0}{R_L}$

$$V_B = V \frac{R_L}{R + R_L} < V_z$$

$$\Rightarrow V < V_z \left(1 + \frac{R}{R_L}\right) \quad / \quad \boxed{V_z < V < V_z \left(1 + \frac{R}{R_L}\right)}$$

$$\frac{V}{V_z} < 1 + \frac{R}{R_L} \quad \frac{R}{R_L} > \frac{V}{V_z} - 1$$

$$\boxed{R > R_L \left(\frac{V}{V_z} - 1\right)}$$



→ always positive because  $V > V_z$

Problem 5a)

$$V_G = V_0 + v_y$$

$$V_0 V_0 = V_0 + v_d$$

$$V_S + V_S = V_S + v_s$$

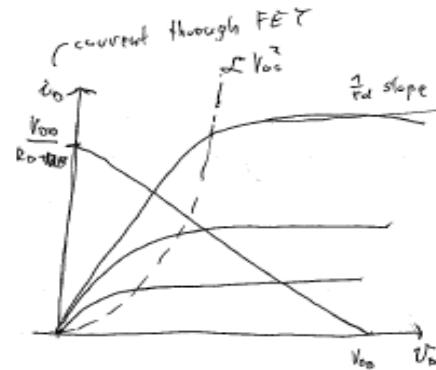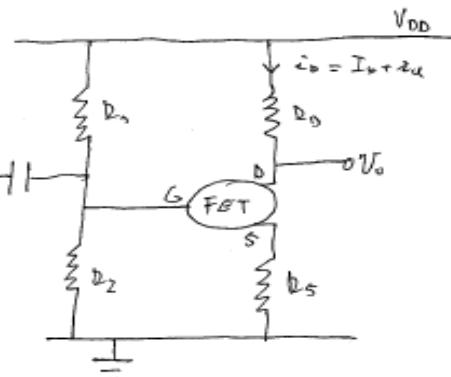

If  $V_{DS} > V_T$  then  $I_D = I_D(V_{DS})$

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2}$$

for biasing

$$\rightarrow v_y = v_i$$

small signal

When  $V_{DS} > V_T$ , transistor conducts

$\rightarrow$  through  $R_D$  and  $R_S$      $I_D = \frac{V_{DD}}{R_D + R_S}$

$$I_D = \frac{V_{DD}}{R_D + R_S} \rightarrow V_S = 0 + I_D R_S = V_{DD} \frac{R_S}{R_D + R_S}$$

$$i_D = i_D(V_{GS}, V_{DS}) = i_D(V_{GS}, V_{DS}) + \frac{\partial i_D}{\partial V_{GS}} v_{GS} + \frac{\partial i_D}{\partial V_{DS}} v_{DS} + \dots$$

Follows from  
Taylor expansion

$$i_D = I_D + g_m v_{GS} + \frac{1}{R_D} v_{DS}$$


$$v_{GS} = v_y - v_x = v_i - i_D R_S$$

$$v_{DS} = v_d - v_x = v_d - i_D R_S$$

$i_D =$

$$\frac{\partial i_D}{\partial V_{GS}} = k(V_{GS} - V_T) \text{ is a constant } g_m$$

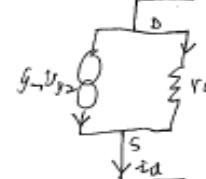comes from  $i_D(V_{GS}) = \frac{k}{2} (V_{GS} R_S - V_T)^2$




we can model this by equivalent

comes from the slope of the saturation region in  $i_D(V_{GS})$  characteristic

$v_i$  affects  $i_D$  by  $g_m v_{GS}$  which affects  $v_{DS}$  which affects back  $i_D \rightarrow$  that's the motivation for both terms  $\frac{\partial i_D}{\partial V_{GS}}$  and  $\frac{\partial i_D}{\partial V_{DS}}$

probably meant  $D_3$

Problem 5 b)

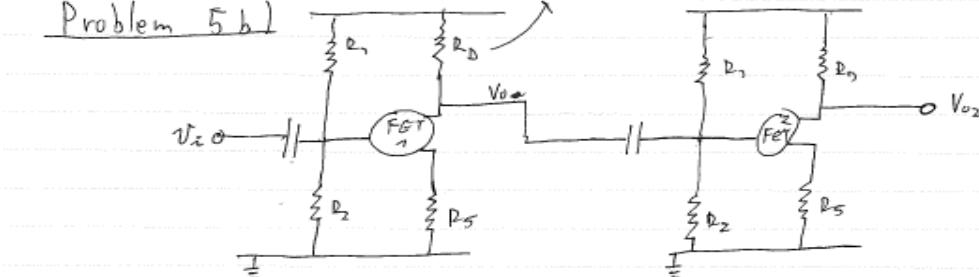


$$G_1 = G_2$$

$\frac{v_{o2}}{v_i} = \frac{v_{o2}}{v_{o1}} \cdot \frac{v_{o1}}{v_i}$  / Two transistor circuits are identical, so the gains are the same  $G = G_1 \cdot G_2 = G^2$

$$G = \frac{v_o}{v_i}$$

we use small signal analysis:

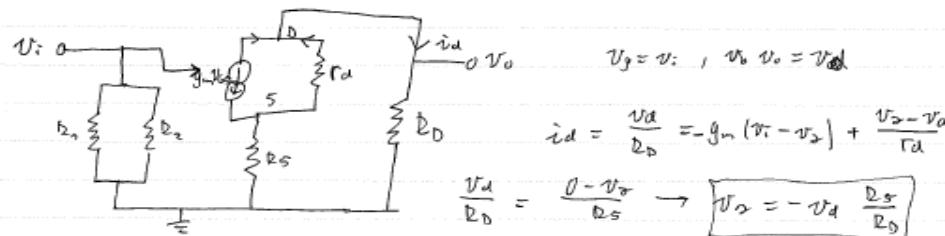

$$v_d = v_i, v_o = v_d$$

$$i_d = \frac{v_d}{R_D} = -g_m(v_i - v_o) + \frac{v_o - v_d}{R_D}$$

$$\frac{v_d}{R_D} = \frac{0 - v_o}{R_S} \rightarrow \boxed{v_o = -v_d \frac{R_S}{R_D}}$$

$$v_d = -g_m D_D v_i + g_m D_D v_o + v_o \frac{R_D}{r_a} - v_o v_d \frac{R_D}{r_d}$$

$$v_d \left( 1 + \frac{R_D}{r_d} \right) = -g_m D_D v_i - v_o \left( \frac{D_D}{r_d} - v_o D_S \left( g_m + \frac{1}{r_d} \right) \right)$$

$$v_o \left( 1 + \frac{R_D}{r_d} + g_m D_S + \frac{1}{r_d} \right) = -g_m D_D v_i$$

$$\boxed{\frac{v_o}{v_i} = \frac{-g_m D_D}{1 + g_m D_S + \frac{R_D + D_S}{r_d}}}$$

$$G = \left( \frac{v_o}{v_i} \right)^2 = \frac{\left( g_m D_D \right)^2}{\left( 1 + g_m D_S + \frac{R_D + D_S}{r_d} \right)^2}$$

for  $r_d \gg D_S, D_D$   
 $g_m D_S \gg 1$

$$\frac{v_o}{v_i} = \frac{-g_m D_D}{1 + g_m D_S + \frac{D_D + D_S}{r_d}} = -\frac{D_D}{D_S} \rightarrow \boxed{G = \left( \frac{D_D}{D_S} \right)^2}$$