

Final exam
Electronics & Signal processing
10-04-2015


Prof. Dr. G. Palasantzas

Grade of written exam:
Points scored from each problem can give you
total max: 10

Georg Simon Ohm



Problem 1 (2 points)

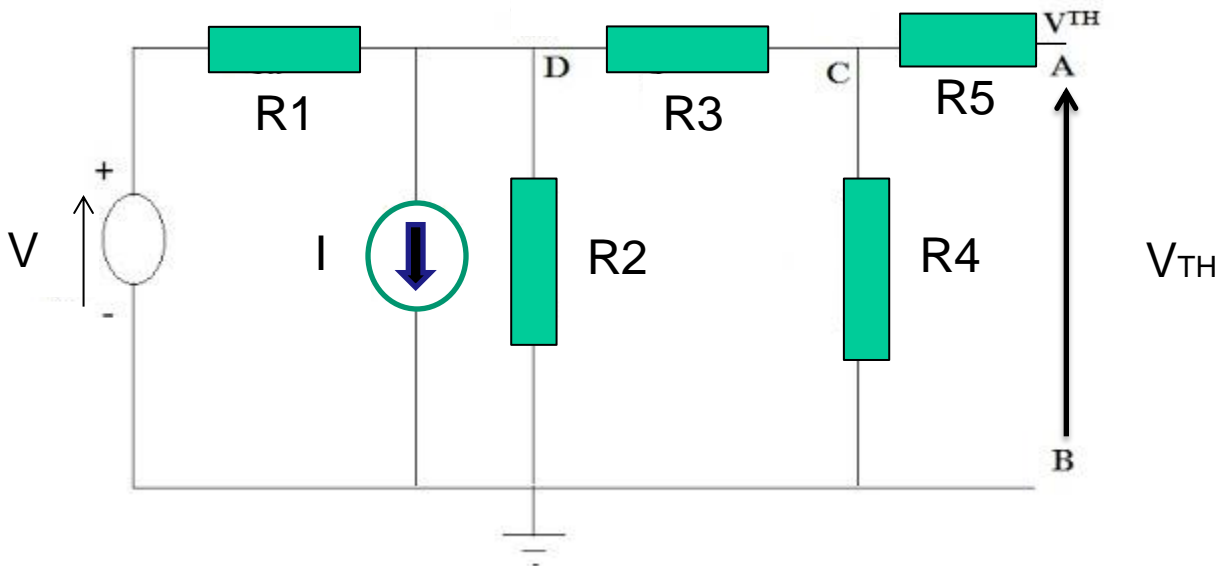


(a: 1.5 points) Derive the Thévenin equivalent between points A and B by calculating the potential V_{TH} (1 point) and R_{TH} (0.5 points) using only the Thevenin-Norton concepts to analyze the circuit.

(b: 0.5 points) If you connect a resistor R_L across the terminals A and B then calculate the current that flows through the resistor R_L .

Problem 2 (2 points)

Ideal opamp: $V_+ = V_-$

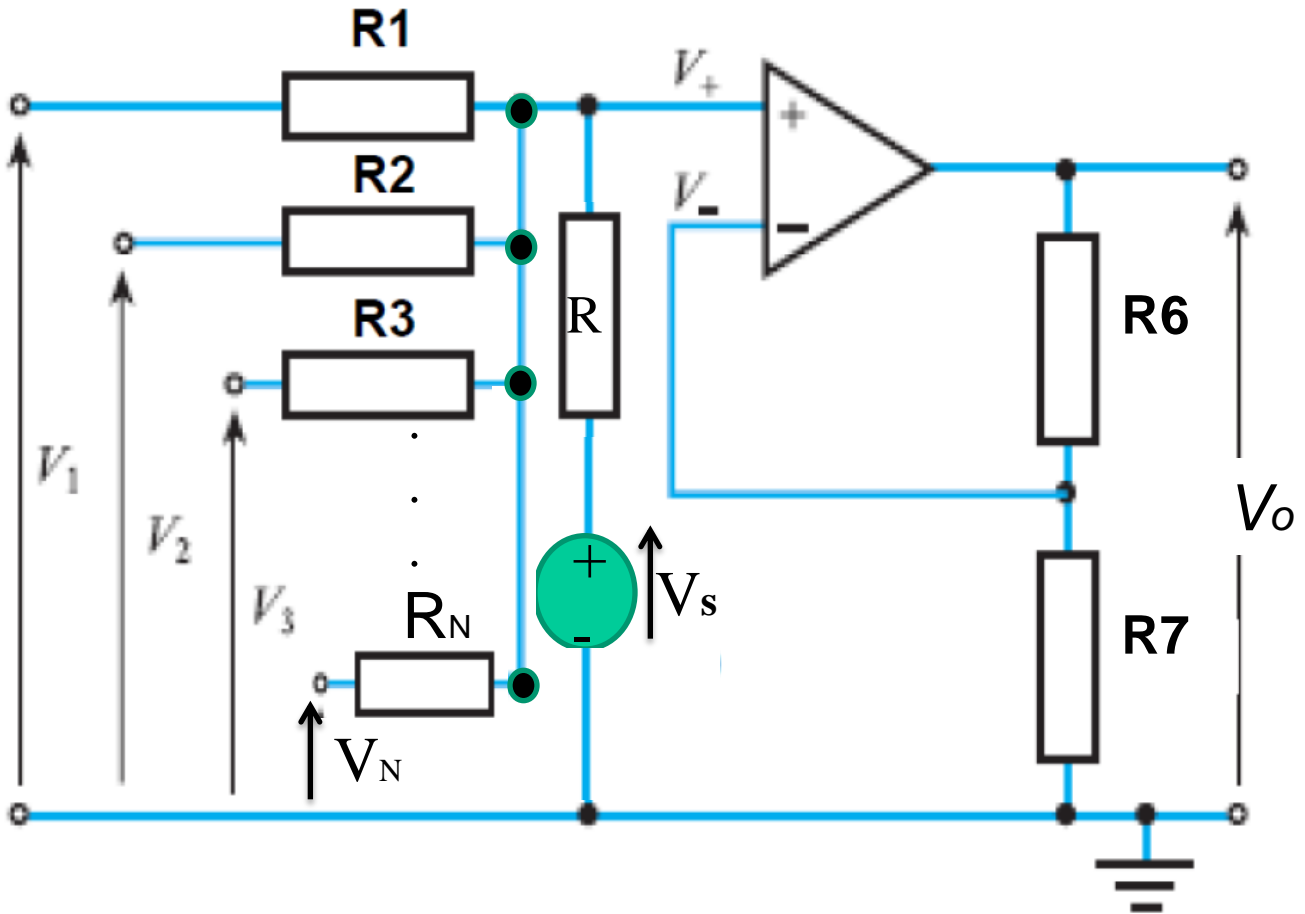


Consider a circuit with input of N voltage sources V_i ($i=1, 2, \dots, N$). The resistor R is connected to the input of the ideal opamp and to an additional voltage source V_s .

- (a) Calculate the potential V_+ (1 point) as a function of the potentials V_i ($i=1 \dots N$), V_s and the resistors R_i ($i=1 \dots N$) and R .
- (b) Calculate the output voltage V_o as a function of the V_i 's, V_s , and the resistors of the opamp circuit shown above (1 point).

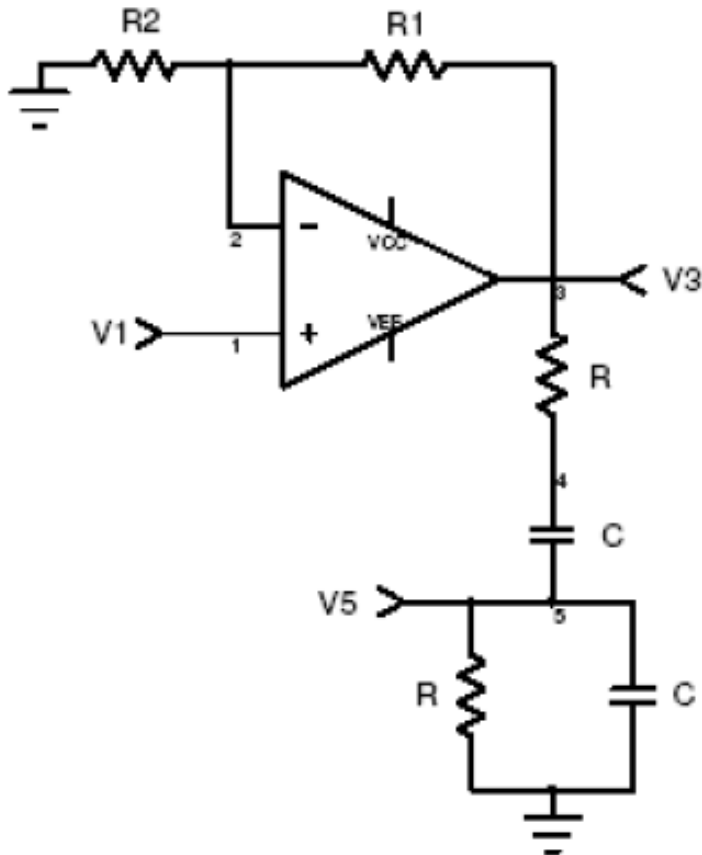Problem 3 (1.5 points)


Consider the circuit (Wien bridge oscillator):




- (a) Calculate the transfer ratio $A = V_3/V_1$ ($V_+ = V_-$; 0.5 points)
- (b) Calculate the transfer ratio $B = V_5/V_3$ and derive the value of ωRC for which B is real (0.5 points)?
- (c) For what value of R_1 / R_2 is $AB = 1$ in order to establish an oscillator by connecting points 1 and 5 (0.5 points) ?.

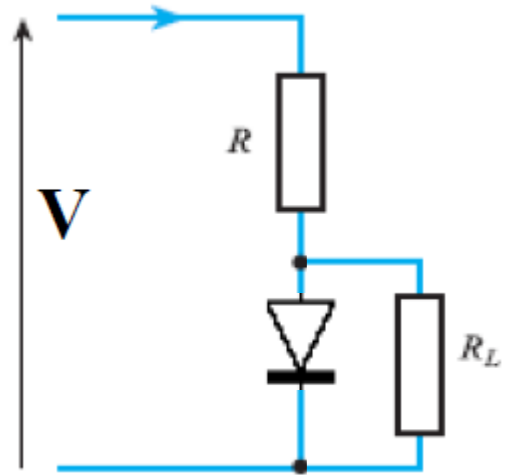Problem 4 (1.5 points)

(a:0.5 points) The diode is ideal with forward conduction voltage V_c . Calculate the current through the resistor R_L assuming the supply voltage is $V > 0$.



(b)

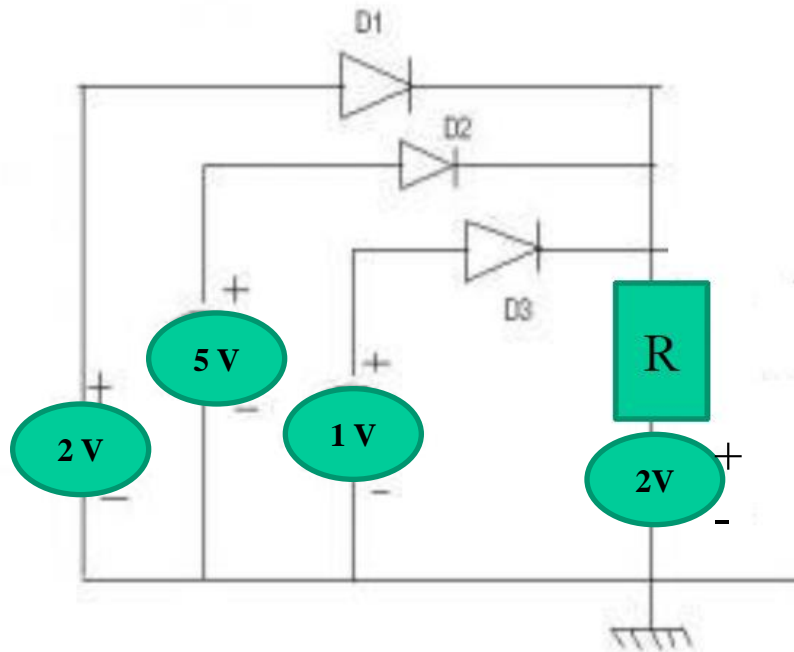

(b1: 0.5 point) Find which diode conducts current [the diodes D_i ($i=1,2,3$) are ideal with voltage for forward conduction $V_c=0.5$ V]. Explain briefly your answer.

(b2: 0.5 point) After you answer point (b1) calculate the current via the resistor R .

Problem 5 (1.5 points)

Design a synchronous counter that goes through the states (use J-K flip flops) 0, 1, 2, 4, 5, 6 shown below:

	<u>Before state</u>			<u>After state</u>		
	Q3	Q2	Q1	Q3	Q2	Q1
0	0	0	0			
1	0	0	1			
2	0	1	0			
4	1	0	0			
5	1	0	1			
6	1	1	0			


Q_{n-1}	Q_n	J	K
0	0	0	*
0	1	1	*
1	0	*	1
1	1	*	0

J	K	Q_n
0	0	Q_{n-1}
0	1	0
1	0	1
1	1	$\overline{Q_{n-1}}$

***: don't care**

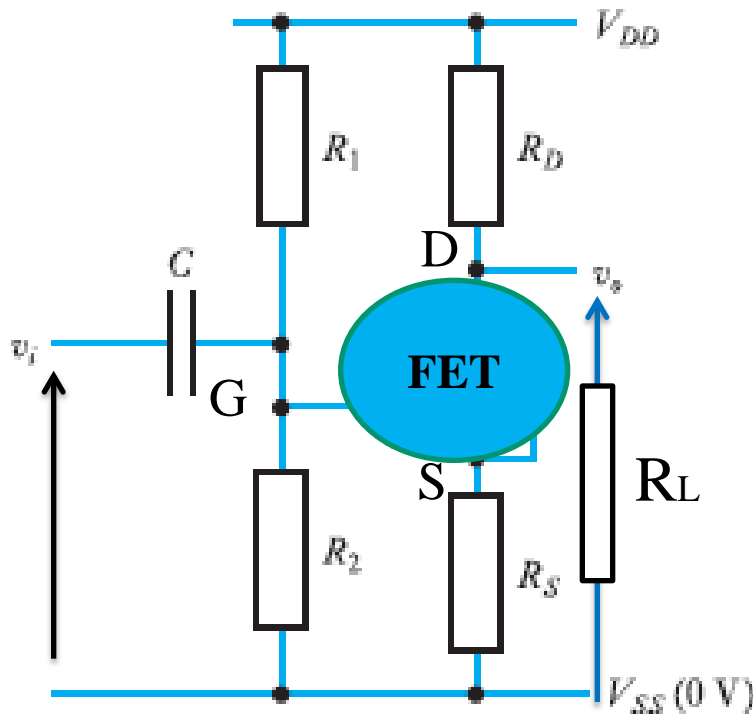Problem 6 (1.5 points)

Application of a small varying input signal v_i leads to small variation of the gate (G), drain (D), and source (S) potentials of the FET shown below:



$$V'_G = V_G + v_g$$

$$V'_D = V_D + v_d$$

$$V'_S = V_S + v_s$$

If we connect a load resistor R_L at output of the drain D (and the ground $V_{SS}=0$), then show that the amplification ratio v_o/v_i , with v_o the variation of the output potential, is given by:

$$\frac{v_o}{v_i} = - \frac{g_m (R_D // R_L)}{1 + g_m R_S + [(R_D // R_L + R_S) / r_d]}$$

with g_m the transconductance and r_d the differential resistance of the FET at saturation.