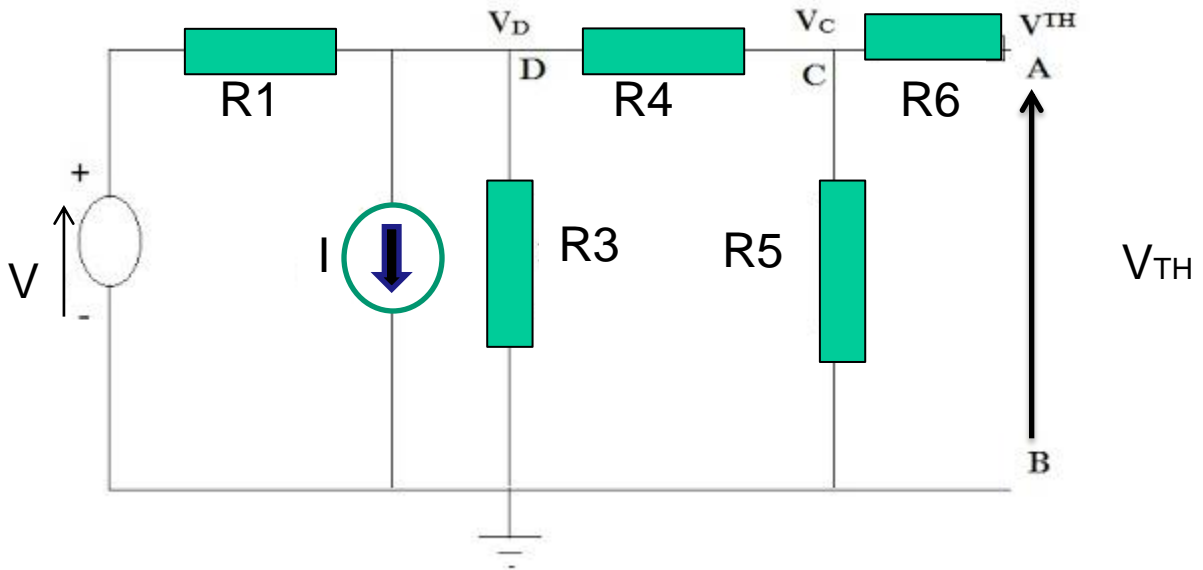


**Final exam
Solutions**




Problem 1 (2 points)




(a: 1.5 points) Give the Thévenin equivalent between A and B by calculating V_{TH} (1 point) and R_{TH} (0.5 points) using only the Thevenin-Norton concepts to analyze this problem.

(b: 0.5 points) If you connect a resistor R_L across the terminals A and B then calculate the current that flows through this resistor.

Solution

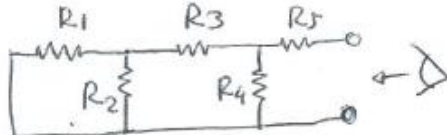
(a) $R_{TH} = ?$  (0.5 points)

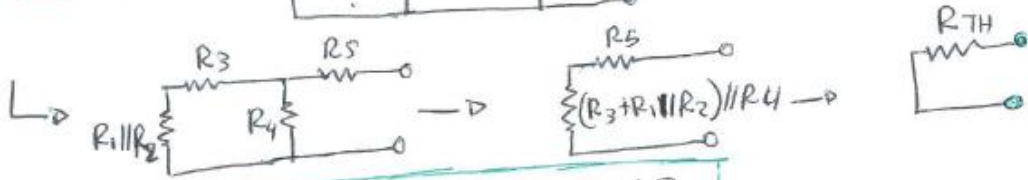

$$R_{TH} = R_5 + R_4 \parallel [R_3 + (R_1 \parallel R_2)]$$


$V_{TH} = ?$

Step 1 :

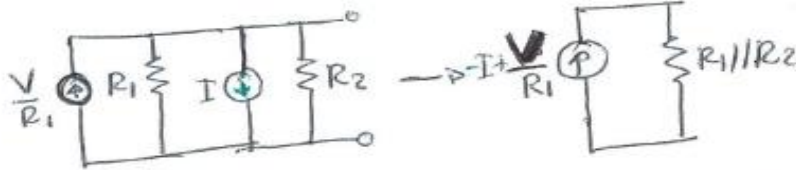


(1 point)



Step 2

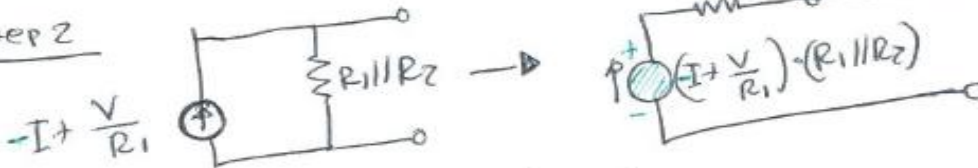

Together with R_3 you have

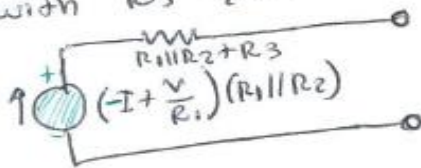


Step 3

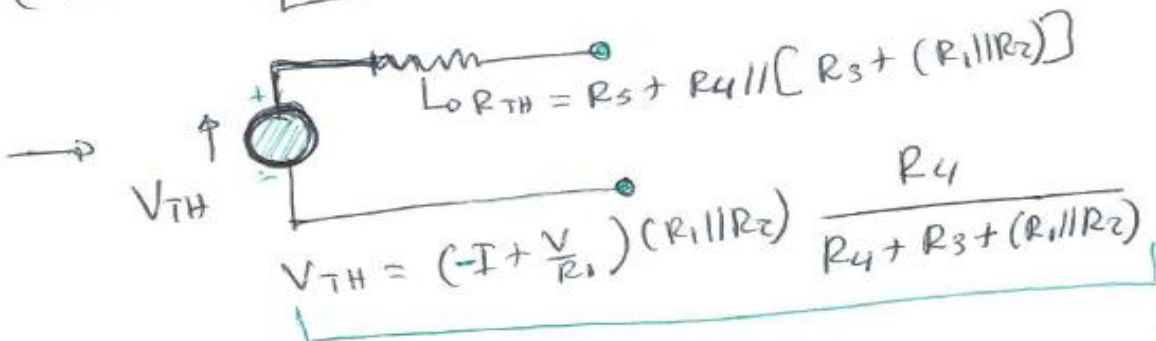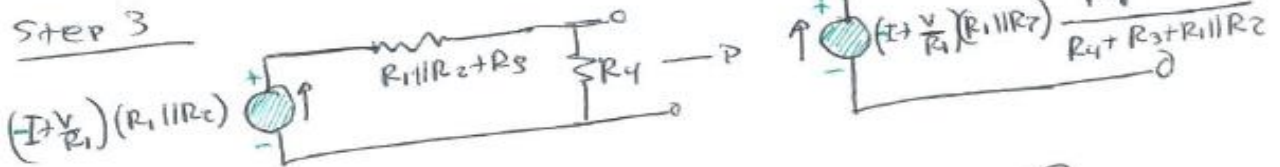

(b) Current through R_L : (0.5 points) $I_L = V_{TH} [1 / (R_L + R_{TH})]$

Problem 2 (2 points)

Ideal opamp: $V_+ = V_-$

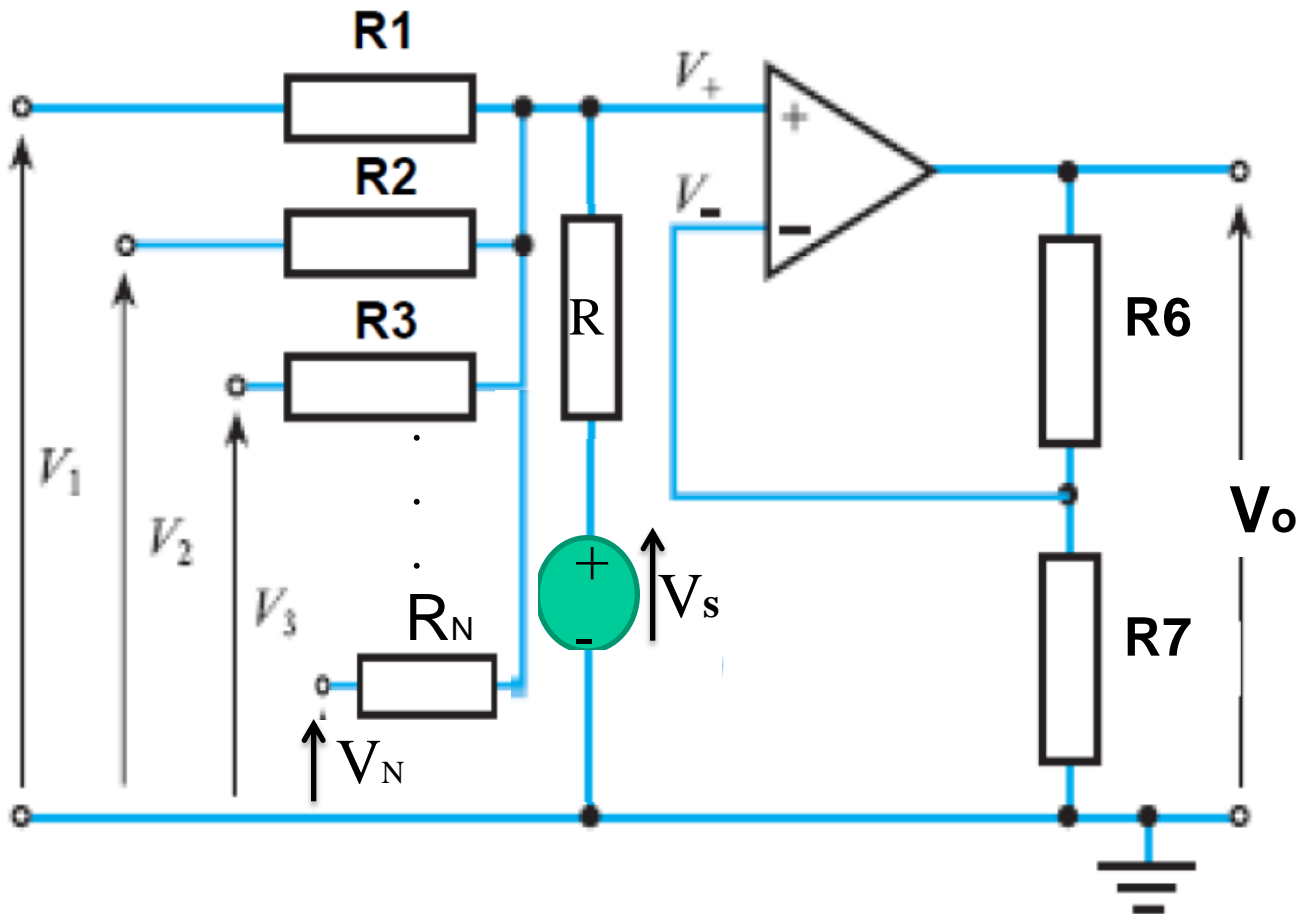

Consider a circuit with input of N voltage sources V_i ($i=1, 2, \dots, N$). The resistor R is connected to the input of the ideal opamp via an additional voltage source V_s .

- (a) Calculate the potential V_+ (1 point)
- (b) Calculate the output voltage V_o as a function of V_i 's, V_s , and the resistors of the circuit shown above (1 point).

Solution

(a) The sum of the currents via V_i 's equals the current that flows via R (K-law 1):

$$\sum_{i=1}^N I_i = I_R \quad (1) \quad I_i = \frac{V_i - V_+}{R_i} \quad (2)$$

$$I_R = \frac{V_+ - V_S}{R} \quad (3)$$

$$(1,2,3) \Rightarrow \sum_{i=1}^N \frac{V_i - V_+}{R_i} = \frac{V_+ - V_S}{R} \Rightarrow$$

$$V_+ \left(\sum_{i=1}^N \frac{1}{R_i} + \frac{1}{R} \right) = \sum_{i=1}^N \frac{V_i}{R_i} + \frac{V_S}{R} \Rightarrow$$

$$V_+ = \frac{\sum_{i=1}^N \frac{V_i}{R_i} + \frac{V_S}{R}}{\sum_{i=1}^N \frac{1}{R_i} + \frac{1}{R}} \quad (4)$$

$$(b) \quad V_+ = V_- \quad ; \quad V_- = V_0 \frac{R_7}{R_7 + R_6} \quad (5)$$

From (4) & (5) since $V_+ = V_-$ for ideal opamp


We obtain

$$V_0 \frac{R_7}{R_7 + R_6} = \frac{\sum_{i=1}^N \frac{V_i}{R_i} + \frac{V_S}{R}}{\sum_{i=1}^N \frac{1}{R_i} + \frac{1}{R}} \Rightarrow$$

$$V_0 = \left(1 + \frac{R_6}{R_7} \right) \frac{\sum_{i=1}^N \frac{V_i}{R_i} + \frac{V_S}{R}}{\sum_{i=1}^N \frac{1}{R_i} + \frac{1}{R}}$$

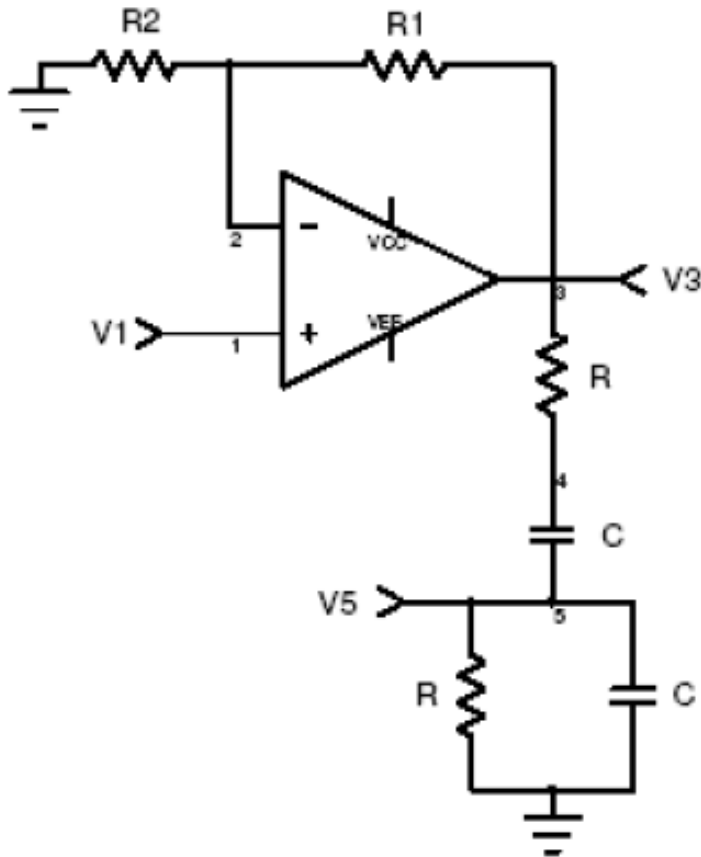Problem 3 (1.5 points)

Consider the circuit (Wien bridge oscillator):



- (a) Calculate the transfer ratio $A=V_3/V_1$ ($V_+=V_-$; 0.5 points)
- (b) Calculate the transfer ratio $B=V_5/V_3$. For what value of ωRC is B real (0.5 points)?
- (c) For what value of R_1 / R_2 is $AB = 1$? (0.5 points).

Solution

(a) $V_+ = V_1$, $V_- = V_3 \{R_2 / [R_2 + R_1]\}$ (voltage divider)
 $V_+ = V_- \rightarrow V_1 = V_3 \{R_2 / [R_2 + R_1]\} \rightarrow A = V_3 / V_1 = 1 + (R_1 / R_2)$

(b) In the more general case we have:

$$\frac{V_5}{V_3} = \frac{Z_2}{Z_1 + Z_2}$$


$$Z_1 = R + \frac{1}{j\omega C} = \frac{j\omega RC + 1}{j\omega C}$$

$$\frac{1}{Z_2} = \frac{1}{R} + j\omega C = \frac{1 + j\omega RC}{R} \rightarrow Z_2 = \frac{R}{1 + j\omega RC}$$

$$\frac{V_5}{V_3} = \frac{\frac{R}{1 + j\omega RC}}{\frac{j\omega RC + 1}{j\omega C} + \frac{R}{1 + j\omega RC}} = \frac{R}{\frac{1 + 2j\omega RC - \omega^2 R^2 C^2}{j\omega C} + R} = \frac{j\omega CR}{1 - \omega^2 R^2 C^2 + 3j\omega RC}$$

$$= \frac{1}{\frac{1 - \omega^2 R^2 C^2}{j\omega RC} + 3} = \frac{1}{3 - j \frac{1 - \omega^2 R^2 C^2}{\omega RC}}$$

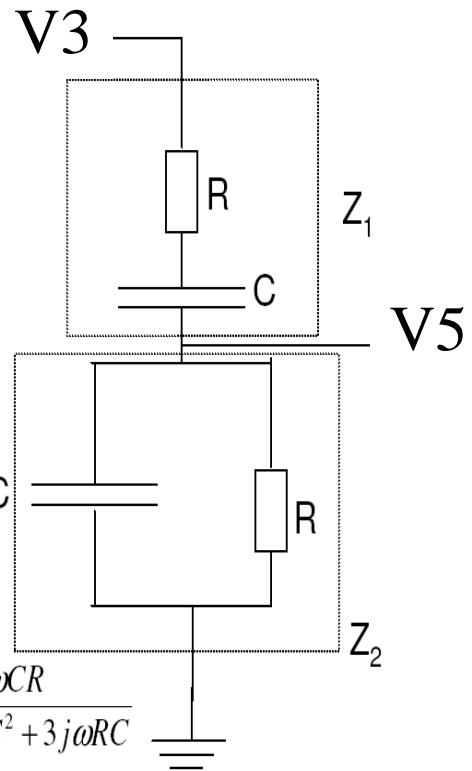For $\omega = 1/RC$ $B = V_5 / v_3$ is real $\rightarrow B = 1/3$




(c) $AB = 1$, since $B = 1/3 \rightarrow A = 3 \rightarrow R_1 / R_2 = 2$


Under these conditions we have formed the Wien Oscillator

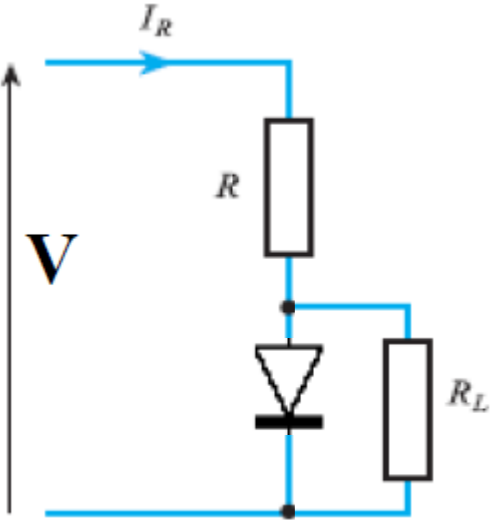Problem 4 (1.5 points)

(a:0.5 points) The diode is ideal with forward conduction voltage V_c . Calculate the current through the resistor R_L .



(b)

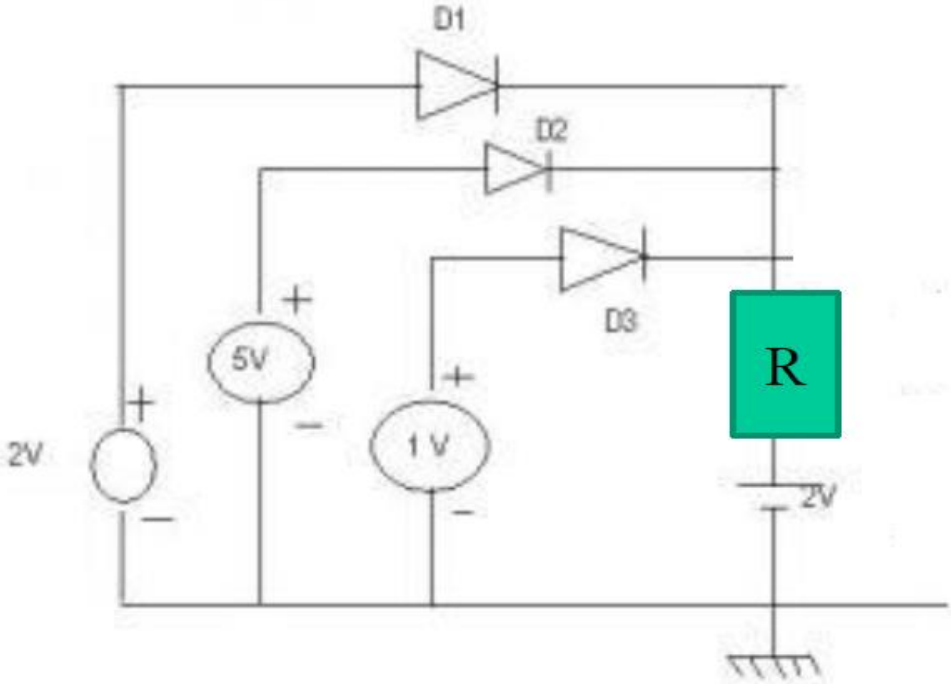

(b1: 0.5 point) Find which diode conducts current [the diodes D_i ($i=1,2,3$) are ideal with voltage for forward conduction $V_c=0.5 V$].

(b2: 0.5 point) Calculate current via the resistor R

Solution

(α)

Define $V_L = V \frac{R_L}{R+R_L}$ the potential on R_L if the diode is absent.

● If $V_L < V_c \Rightarrow$ Diode is not conducting \Rightarrow P

$$I_{R_L} = V / (R + R_L)$$

● If $V_L \geq V_c \Rightarrow$ Diode is conducting \Rightarrow P

$$I_{R_L} = \frac{V_c}{R_L}$$

b1) Only D2 conducts. This is because if we denote with V the three input voltages (1, 2, 5 V) then the voltage difference $V-2$ only for D2 is larger than V_c ($V-2 > V_c$) to support forward conduction. (1 point)

b2) $I = [(5 - V_c) - 2] / R = 2.5 / R$ (1 point)

Problem 5 (1.5 points)

Design a synchronous counter that goes through the states (use J-K flip flops) 0, 1, 2, 4, 5, 6 shown below:

<u>Before state</u>			<u>After state</u>		
Q3	Q2	Q1	Q3	Q2	Q1
0	0	0			
0	0	1			
0	1	0			
1	0	0			
1	0	1			
1	1	0			

Q_{n-1}	Q_n	J	K
0	0	0	*
0	1	1	*
1	0	*	1
1	1	*	0


***: don't care**

J	K	Q_n
0	0	Q_{n-1}
0	1	0
1	0	1
1	1	$\overline{Q_{n-1}}$

Solution


<u>Before state</u>			<u>After state</u>			<u>Flip-Flop Inputs</u>					
Q3	Q2	Q1	Q3	Q2	Q1	J3	K3	J2	K2	J1	K1
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X
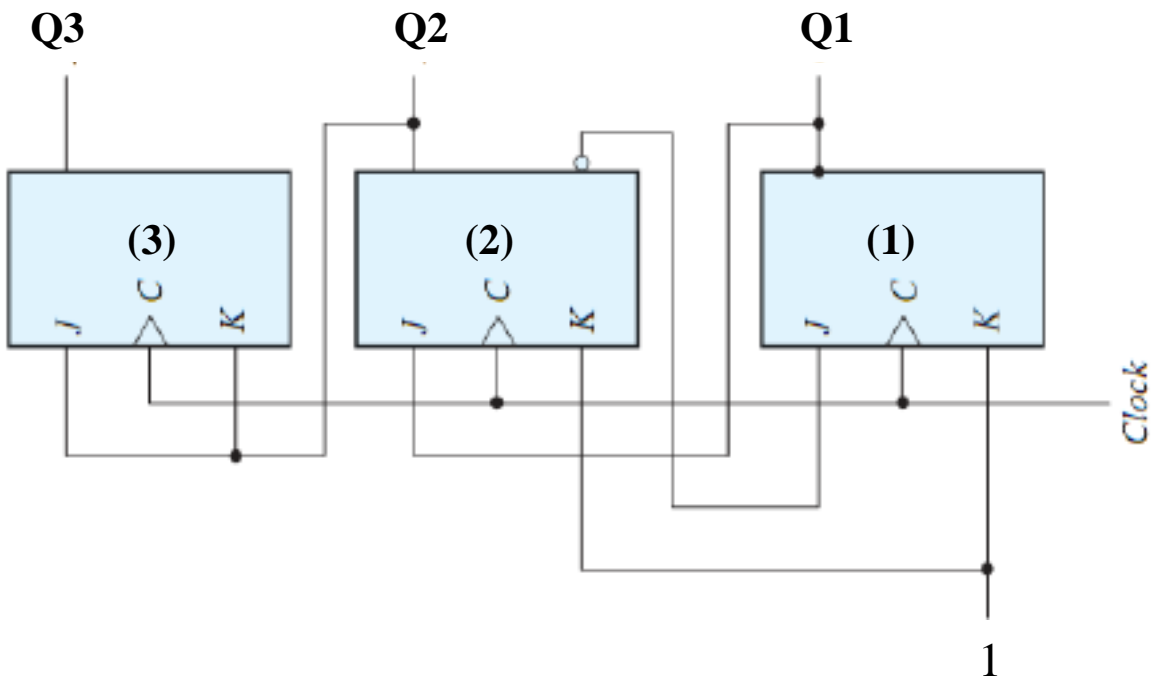
$$J3=K3=Q2, \quad J2=Q1, \quad K2=1, \quad J1=\overline{Q2}, \quad K1=1$$



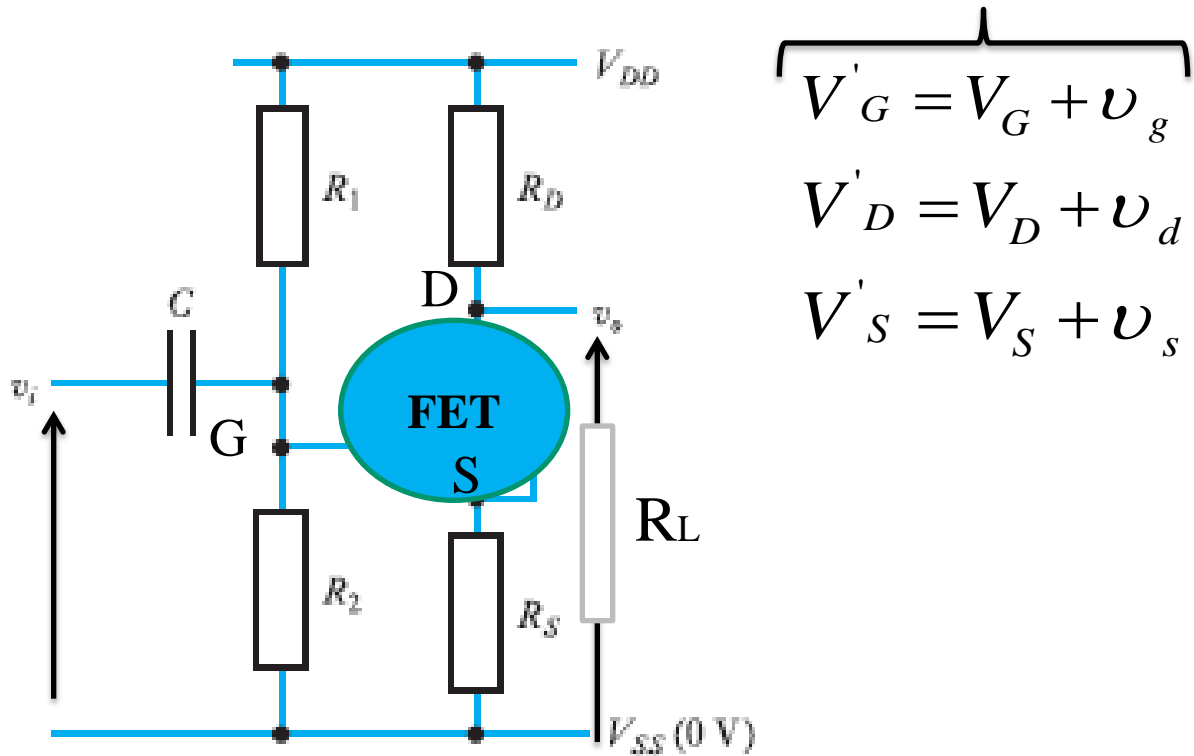Problem 5 (1.5 points)

An application of a small varying input signal v_i leads to small variation of the gate, drain, and source potentials :




If we connect a load resistor R_L at output of the drain D (and the ground $V_{SS}=0$), then show that the amplification ratio v_o/v_i is given by:

$$\frac{v_o}{v_i} = - \frac{g_m (R_D // R_L)}{1 + g_m R_S + [(R_D // R_L + R_S) / r_d]}$$

Solution

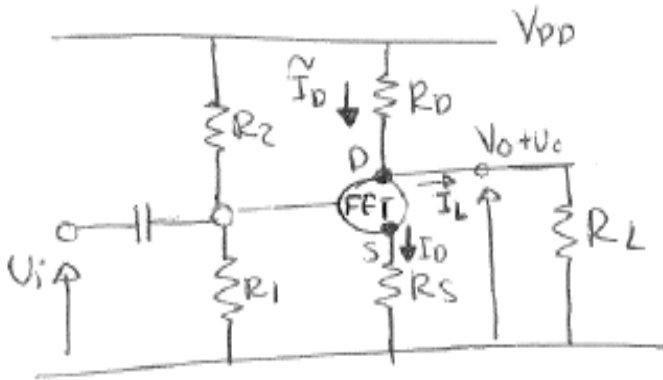(1-method: first principles analysis) *This is only for tough cookies!*



$$U_g \equiv U_i$$

$$U_o \equiv U_d$$

$$i_d = g_m(U_g - U_s) + \frac{U_d - U_s}{r_d}$$

$$\tilde{I}_D = I_D + I_L \quad (1)$$

$$V_o = V_{DD} - \tilde{I}_D \cdot R_D \Rightarrow \text{take a variation} \Rightarrow \delta V_o = U_o = \delta V_{DD} - \delta \tilde{I}_D \cdot R_D \Rightarrow \delta \tilde{I}_D = i_d + i_L$$

$$U_o = - (i_d + i_L) R_D \quad (2)$$

$$V_o = I_L \cdot R_L \Rightarrow \delta V_o = U_o = \frac{\delta I_L \cdot R_L}{I_L} = p$$

$$U_o = i_L \cdot R_L \Rightarrow i_L = U_o / R_L \quad (3)$$

$$(2) \text{ \& } (3) \Rightarrow U_o = - i_d R_D - U_o \frac{R_D}{R_L} = p$$

$$\Rightarrow U_o \left[1 + \frac{R_D}{R_L} \right] = - i_d R_D \quad (4)$$

We still need to eliminate i_d and the potential U_s

$$(1) \Rightarrow \frac{V_{DD} - V_o}{R_D} = \frac{I_D}{R_S} + \frac{I_L}{R_L}, \text{ take a variation}$$

$$-\frac{\delta V_o}{R_D} = \frac{\delta V_S}{R_S} + \frac{\delta V_o}{R_L} \Rightarrow -\frac{U_o}{R_D} = \frac{U_S}{R_S} + \frac{U_o}{R_L} = p$$

$$\frac{U_S}{R_S} = -U_o \left[\frac{1}{R_D} + \frac{1}{R_L} \right] = p \quad U_S = -U_o \frac{R_S}{R_{DL}}, \quad R_{DL} = R_D \parallel R_L \quad (5)$$

substitute in (4) from (5) the V_s and
 replace also $V_g = V_i$, $V_d = V_o$

$$V_o \left[1 + \frac{R_D}{R_L} \right] = - \left[g_m (V_i + V_o \frac{R_S}{R_{DL}}) + V_o \frac{1 + \frac{R_S}{R_{DL}}}{V_d} \right] R_D$$

$$V_o \left[\frac{1}{R_D} + \frac{1}{R_L} \right] = - g_m V_i - g_m V_o \frac{R_S}{R_{DL}} = V_o \frac{R_{DL} + R_S}{V_d R_{DL}}$$

$$\frac{V_o}{R_{DL}} + g_m V_o \frac{R_S}{R_{DL}} + V_o \frac{R_{DL} + R_S}{V_d R_{DL}} = - g_m V_i \Rightarrow$$

$$V_o \left[1 + g_m R_S + \frac{R_{DL} + R_S}{V_d} \right] \frac{1}{R_{DL}} = - g_m V_i \Rightarrow$$


$$\boxed{\frac{V_o}{V_i} = - \frac{g_m R_{DL}}{1 + g_m R_S + \frac{R_{DL} + R_S}{V_d}}}$$

Although this looks complicated, this is what is happening in reality!

you can extend this approach beyond first order perturbation theory-
 a limitation for method-2 as follows!.

(2-method: small signal circuit) *This is for normal cookies!*

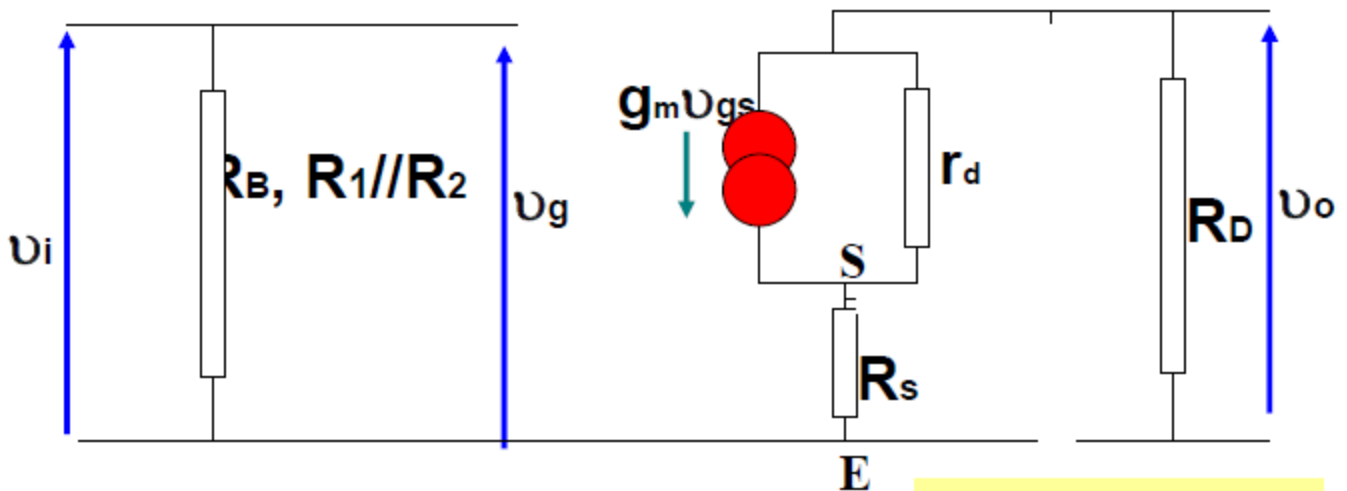Replace in all shown below: R_D with $R_D // R_L$. This is because in this design R_D parallel with R_L



Apply K-law for the current at points S & E

$$g_m v_{gs} + (v_o - v_s) / r_d - v_s / R_s = 0 \quad (\text{S})$$

$$(v_o / R_D) + (v_s / R_s) = 0 \quad (\text{E})$$

$$v_{gs} = v_g - v_s$$

$$g_m v_{gs} + (v_o - v_s) / r_d - v_s / R_s = 0 \quad (S)$$

$$(v_o / R_D) + (v_s / R_s) = 0 \quad (E)$$

$$v_{gs} = v_g - v_s$$



$$v_g = v_i$$

$$\text{Gain: } v_o / v_i = -g_m R_D / [1 + g_m R_s + (R_s + R_D) / r_d]$$

To have the desired result replace : $R_D \rightarrow R_D // R_L$