

Final exam
Electronics & Signal processing
06-04-2016


Prof. Dr. G. Palasantzas

Grade of written exam:

Mark is cummulative points scored for all problems

Total maximum score : 10


Problem 1 (1.5 points)

 

Derive the Thévenin equivalent between points A and B by calculating the Thévenin potential V_{TH} (1 point) and the Thévenin resistance R_{TH} (0.5 points) using only the Thevenin-Norton concepts to analyze the circuit.

 Problem 2 (2.5 points)

Consider the circuit below with two ideal opamps ($V_+ = V_-$)



(a: 0.5 points) Show that : $\frac{V(6)}{V(3)} = - \frac{1}{j\omega\tau_3}$

where $\tau_3 = R_3C_3$.

(b: 1.5 points) Show that

$$V(2) = \frac{\left(\frac{R_1}{R_2} + j\omega\tau_1\right) V(3) + V(1)}{1 + \frac{R_1}{R_2} + j\omega\tau_1}$$

where $\tau_1 = R_1C_1$.


(c: 0.5 points) Show that $V(3) = V(4) = \frac{V(2)}{1 + j\omega\tau_2}$

where $\tau_2 = R_2C_2$.

 
Problem 3 (1 point)

The Nyquist diagrams below represent four circuits (0.25 points per circuit). In each case determine:


- the number of low and high-frequency cut-offs
- whether or not the circuit is stable.




(a)

 

(b)

 


(c)

 

(d)

 Problem 4 (1.5 points)


The diodes C_1 and C_2 are assumed ideal with forward conduction voltage $V_c \ll V_{in} (>0)$. The Diode C_2 is also a Zener diode with reverse conduction voltage $V_z (\ll V_{in})$.



Calculate the current through the resistor R_2 and discuss possible restrictions for the resistor ratio R_1/R_2 depending on the operation of C_1 and C_2 .

 Problem 5 (2 points)

(a: 1 point) Using the output table given below, design the synchronous 8-counter 0→7 (X: do not care) using 3 J-K flip-flops:




Output State Transitions			Flip-flop inputs								
Present State			Next State			J2 K2		J1 K1		J0 K0	
Q2	Q1	Q0	Q2	Q1	Q0						
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1

(b: 1 point) Using the result from (a) identify J-K flip-flops acting as internal clocks in order to design a simpler version of the synchronous 8-counter (asynchronous).

Problem 6 (1.5 points)

Consider a FET as shown bellow:

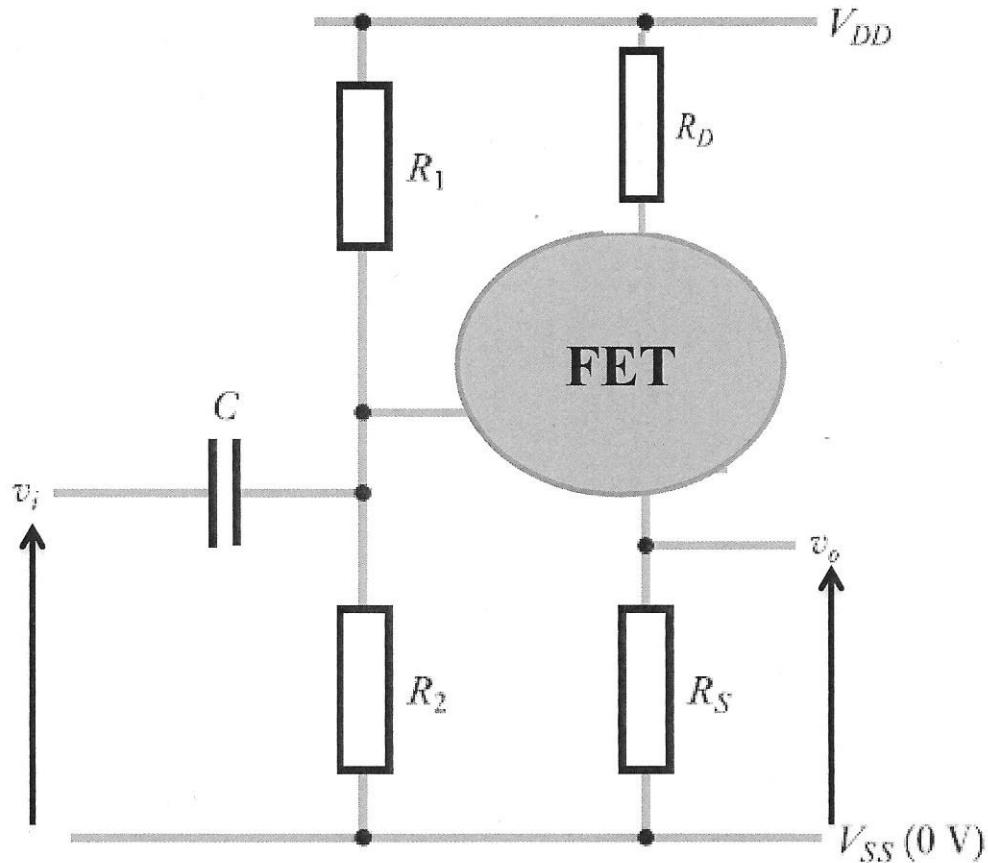

Show that the amplification ratio of the input/output potential variations v_o/v_i is given by:

$$\frac{v_o}{v_i} = \frac{g_m R_S}{1 + g_m R_S + [(R_D + R_S) / r_d]}$$

with g_m the transconductance and r_d the differential resistance of the FET operating at saturation.