

Final exam
Electronics & Signal processing
06-04-2016


Prof. Dr. G. Palasantzas

Grade of written exam:

Mark is cumulative points scored for all problems

Total maximum score : 10


Problem 1 (1.5 points)

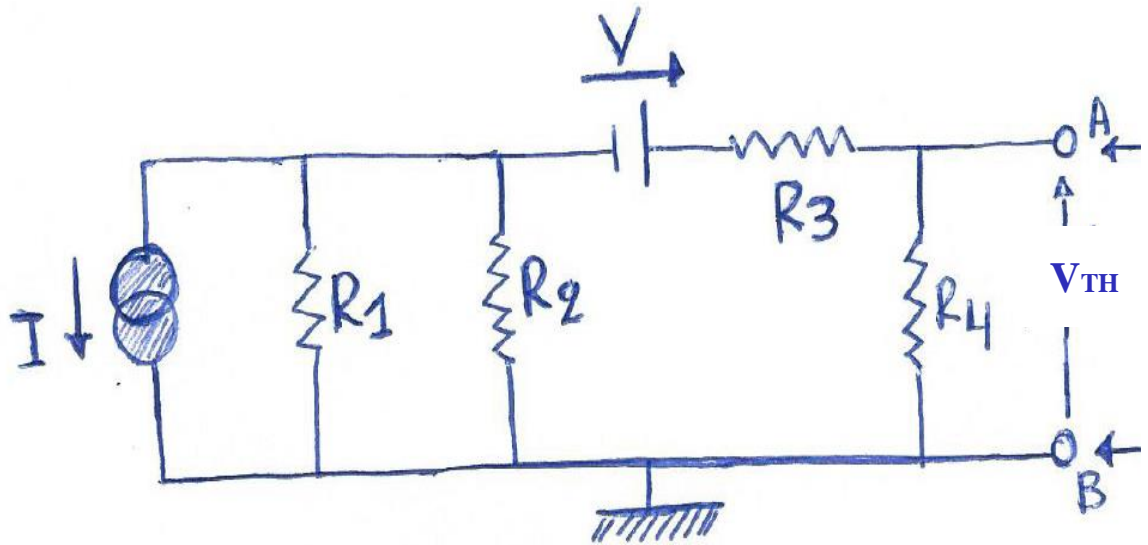

Derive the Thévenin equivalent between points A and B by calculating the Thévenin potential V_{TH} (1 point) and the Thévenin resistance R_{TH} (0.5 points) using only the Thevenin-Norton concepts to analyze the circuit.


Solution Problem 1

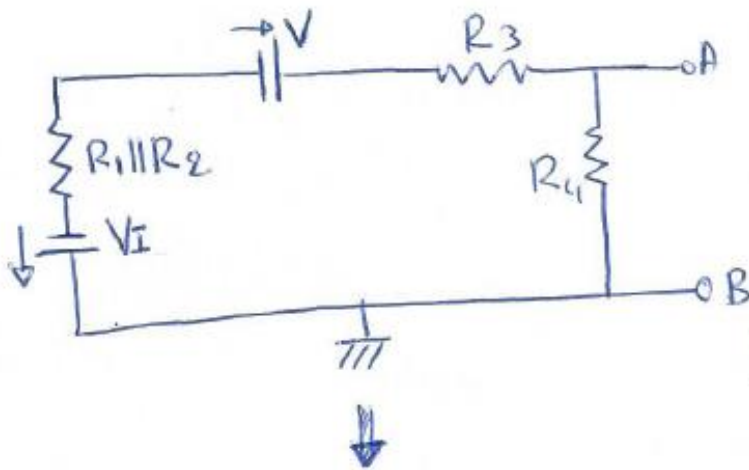Transform first to have only voltage sources




$$V_I = I \cdot (R_1 \parallel R_2)$$
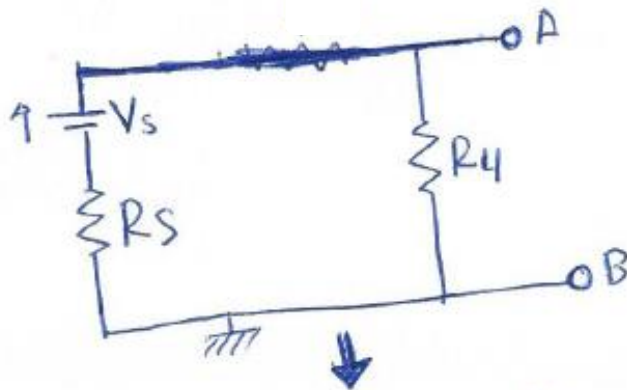
$$\left\{ \begin{aligned} R_1 \parallel R_2 &= \frac{R_1 R_2}{R_1 + R_2} \\ \text{Resistors in parallel} \end{aligned} \right\}$$



$$V_S = V - I (R_1 \parallel R_2)$$

$$R_S = R_3 + R_1 \parallel R_2$$

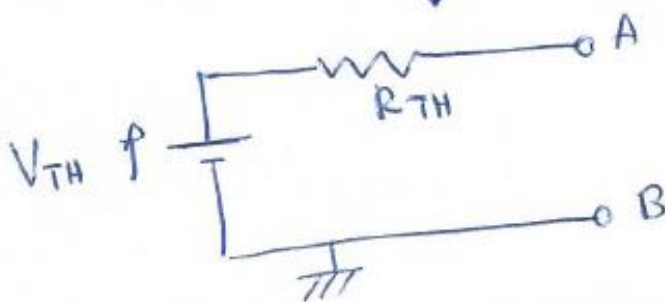

$$V_{TH} = V_S \frac{R_4}{R_S + R_4} = \dots$$


$$V_{TH} = [V - I(R_1 \parallel R_2)] \frac{R_4}{R_S + R_4}$$

$$\Rightarrow V_{TH} = [V - I(R_1 \parallel R_2)] \frac{R_4}{R_3 + R_4 + (R_1 \parallel R_2)} \quad (1 \text{ point})$$

$$R_{TH} = R_S \parallel R_4 = (R_3 + R_1 \parallel R_2) \parallel R_4 \quad (0.5 \text{ points})$$

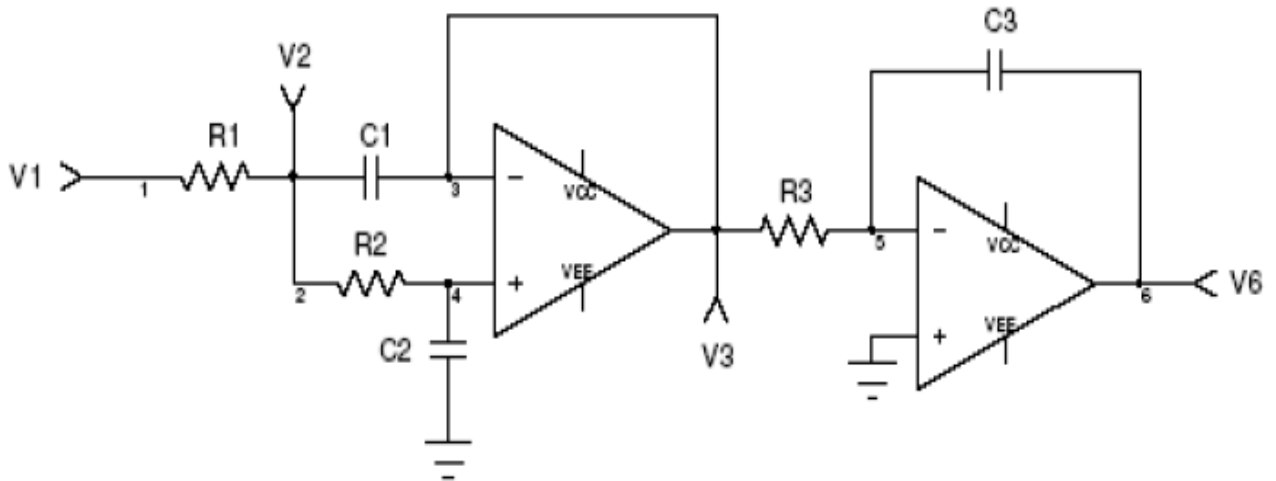Problem 2 (2.5 points)

Consider the circuit below with two ideal op amps ($V_+ = V_-$)



(a: 0.5 points) Show that :
$$\frac{V(6)}{V(3)} = - \frac{1}{j\omega\tau_3}$$

where $\tau_3 = R_3C_3$.

(b: 1.5 points) Show that

$$V(2) = \frac{\left(\frac{R_1}{R_2} + j\omega\tau_1\right) V(3) + V(1)}{1 + \frac{R_1}{R_2} + j\omega\tau_1}$$

where $\tau_1 = R_1C_1$.

(c: 0.5 points) Show that
$$V(3) = V(4) = \frac{V(2)}{1 + j\omega\tau_2}$$


where $\tau_2 = R_2C_2$.

Solution Problem 2


(a)

$$a) \frac{V(3)}{R_3} + \frac{V(6)}{j\omega C_3} = 0$$
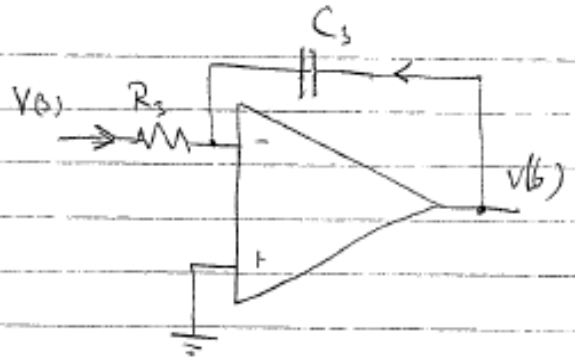
$$\frac{V(6)}{V(3)} = - \frac{1}{j\omega R_3 C_3} = - \frac{1}{j\omega T_3}$$



(b)

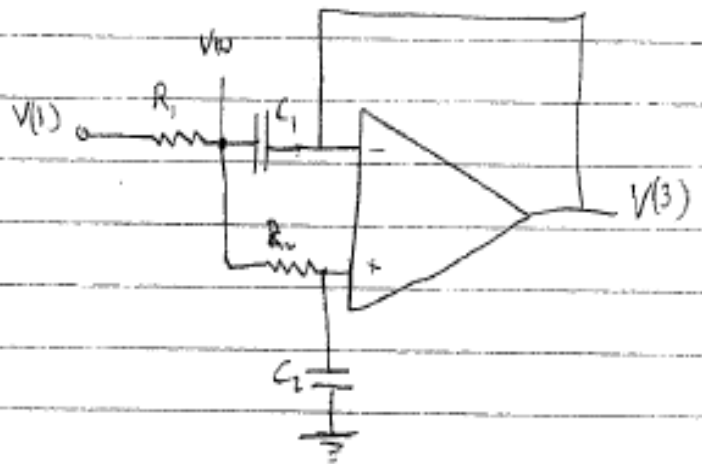

$$V(2) = \frac{\frac{1}{j\omega C_1} // R_2}{R_1 + \frac{1}{j\omega C_1} // R_2} V(1) + \frac{R_1}{R_1 + \frac{1}{j\omega C_1} // R_2} V(3) \text{ (1 point)}$$

$$\frac{1}{j\omega C_1} // R_2 = \frac{\frac{R_2}{j\omega C_1}}{R_2 + \frac{1}{j\omega C_1}} = \frac{-R_2}{1 + j\omega R_2 C_1}$$

$$R_1 + \frac{1}{j\omega C_1} \parallel R_2 = R_1 + \frac{R_2}{1 + j\omega R_2 C_1} = \frac{R_1 + R_2 + j\omega R_2 R_1 C_1}{1 + j\omega R_2 C_1}$$

$$V(2) = \frac{R_2}{R_1 + R_2 + j\omega R_2 R_1 C_1} V(1) + \frac{R_1 + j\omega R_2 R_1 C_1}{R_1 + R_2 + j\omega R_2 R_1 C_1} V(3)$$

$$V(2) = \frac{1}{1 + \frac{R_1}{R_2} + j\omega T_1} V(1) + \frac{\frac{R_1}{R_2} + j\omega T_1}{1 + \frac{R_1}{R_2} + j\omega T_1} V(3)$$

$$V(2) = \frac{\left(\frac{R_1}{R_2} + j\omega T_1\right) V(3) + V(1)}{1 + \frac{R_1}{R_2} + j\omega T_1} \quad (0.5 \text{ points})$$


$$c) \quad V(4) = \frac{1}{R_2 + \frac{1}{j\omega C_2}} V(2) = \frac{1}{1 + j\omega R_2 C_2} V(2)$$

$$\therefore V(3) = V(4) = \frac{1}{1 + j\omega T_2} V(2) \quad T_2 = R_2 C_2$$

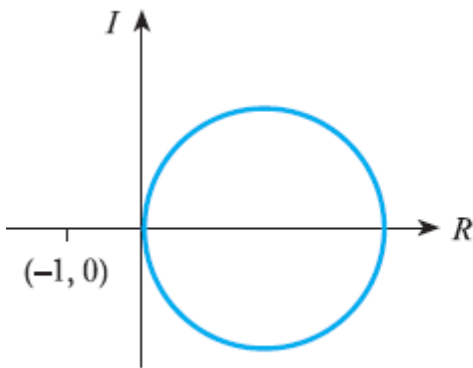
Problem 3 (1 point)

The Nyquist diagrams below represent four circuits (0.25 points per circuit). In each case determine:


- the number of low and high-frequency cut-offs
- whether or not the circuit is stable.




(a)

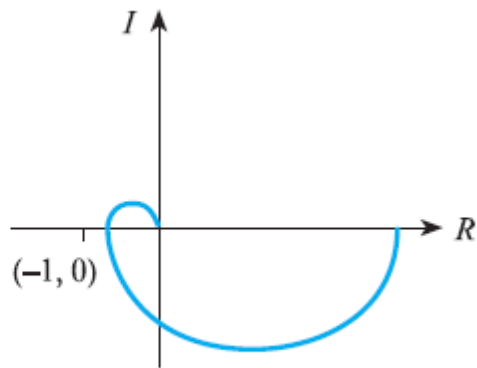

(b)

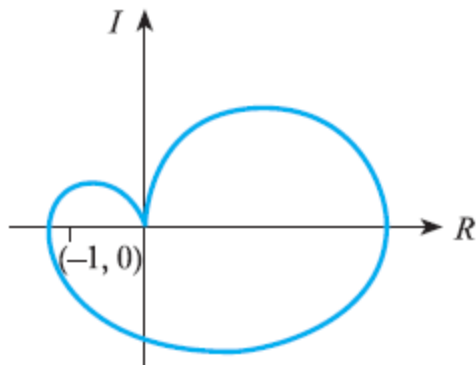

(c)

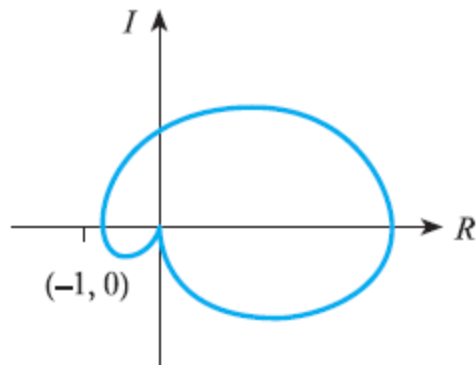

(d)

Solution Problem 3

a) 1 high cut-off
1 low cut-off
stable


b) 3 high cut-offs
stable

c) 3 high cut-offs
1 low cut-off
unstable

d) 1 high cut-off
3 low cut-offs
stable

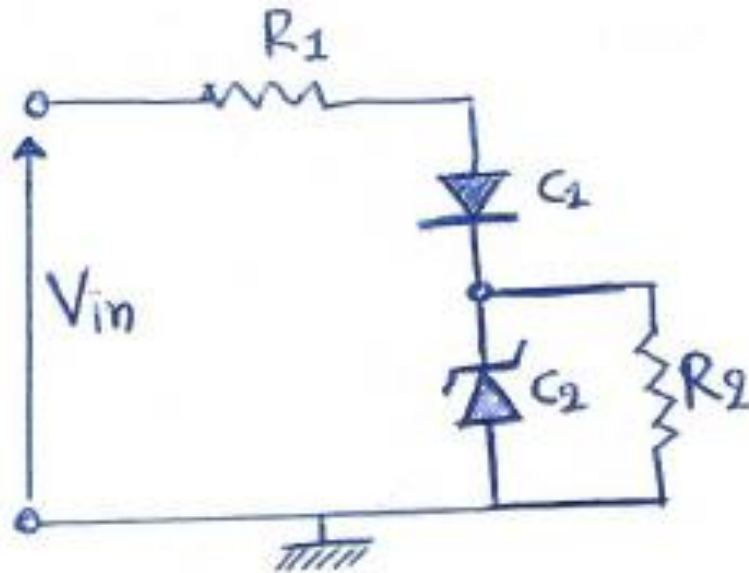
Problem 4 (1.5 points)

The diodes C_1 and C_2 are assumed ideal with forward conduction voltage $V_c \ll V_{in} (>0)$. The Diode C_2 is also a Zener diode with reverse conduction voltage $V_z (\ll V_{in})$.



Calculate the current through the resistor R_2 and discuss possible restrictions for the resistor ratio R_1/R_2 depending on the operation of C_1 and C_2 .

Solution Problem 4

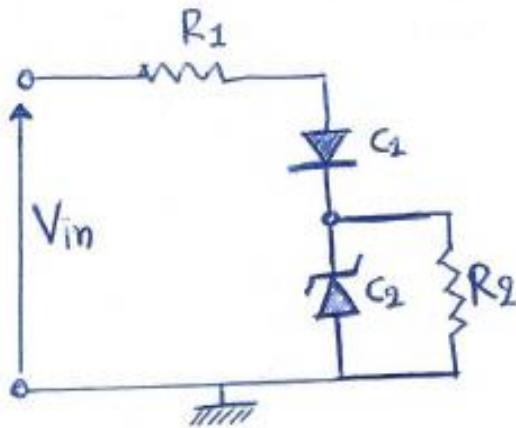

$V_{in} \gg V_c \rightarrow$ Diode C_1 conducts
 C_2 can conduct only as Zener

If we ignore zener C_2 then the potential at point "O" is

$$V_o = V_{in} - V_c - I R_1 \quad (1)$$

$$I = \frac{V_{in} - V_c}{R_1 + R_2} \quad (2)$$

(1) & (2) give $V_o = (V_{in} - V_c) \frac{R_2}{R_1 + R_2} \quad (3)$

(I) If $V_o < V_z$ the diode C_2 is not conducting as a zener \Rightarrow

$I_2 = I = \frac{V_{in} - V_c}{R_1 + R_2} \quad (4)$

(0.5 points)

(II) If $V_0 \geq V_Z$ then the zener is conducting and the potential at point o is $V_Z \Rightarrow$

$$I_Z = \frac{V_Z}{R_2} \quad (5) \quad (0.5 \text{ points})$$

since $V_0 \geq V_Z \Rightarrow (V_{in} - V_C) \frac{R_2}{R_1 + R_2} \geq V_Z \Rightarrow$

$$\frac{R_1}{R_2} + 1 \leq \frac{V_{in} - V_C}{V_Z} \Rightarrow$$


$$\boxed{\frac{R_1}{R_2} \leq \frac{V_{in} - V_C}{V_Z} - 1} \quad (6) \quad (0.5 \text{ points})$$

Restriction for R_1/R_2

If (6) is not valid then the zener is not conducting!

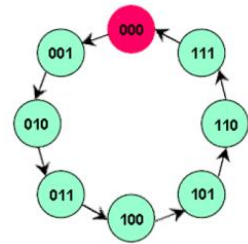Problem 5 (2 points)

(a: 1 point) Using the output table given below, design the synchronous 8-counter $0 \rightarrow 7$ (X: do not care) using 3 J-K flip-flops:



0


Output State Transitions			Flip-flop inputs								
Present State			Next State			J2 K2		J1 K1		J0 K0	
Q2	Q1	Q0	Q2	Q1	Q0						
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1

(b: 1 point) Using the result from (a) identify J-K flip-flops acting as internal clocks in order to design a simpler version of the synchronous 8-counter $0 \rightarrow 7$ (asynchronous)

(a)


Output State Transitions			Flip-flop inputs		
Present State		Next State	J2 K2	J1 K1	J0 K0
Q2	Q1	Q0	Q2	Q1	Q0
0	0	0	0 X	0 X	1 X
0	0	1	0 X	1 X	X 1
0	1	0	0 X	X 0	1 X
0	1	1	1 X	X 1	X 1
1	0	0	X 0	0 X	1 X
1	0	1	X 0	1 X	X 1
1	1	0	X 0	X 0	1 X
1	1	1	X 1	X 1	X 1

Solution Problem 5

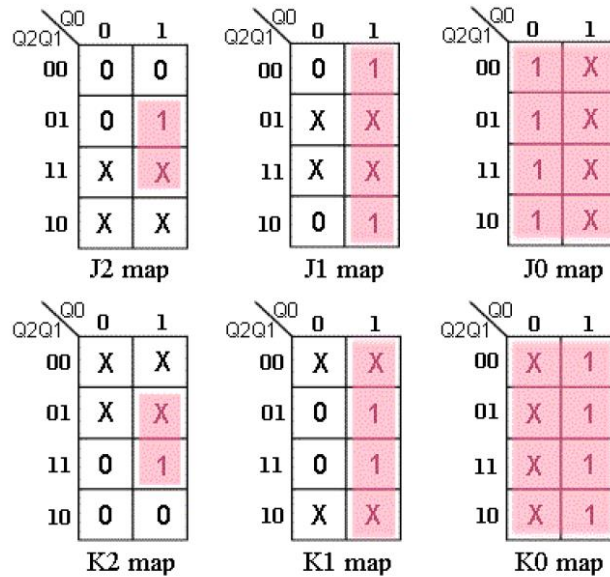

The K-maps for J-Ks are:

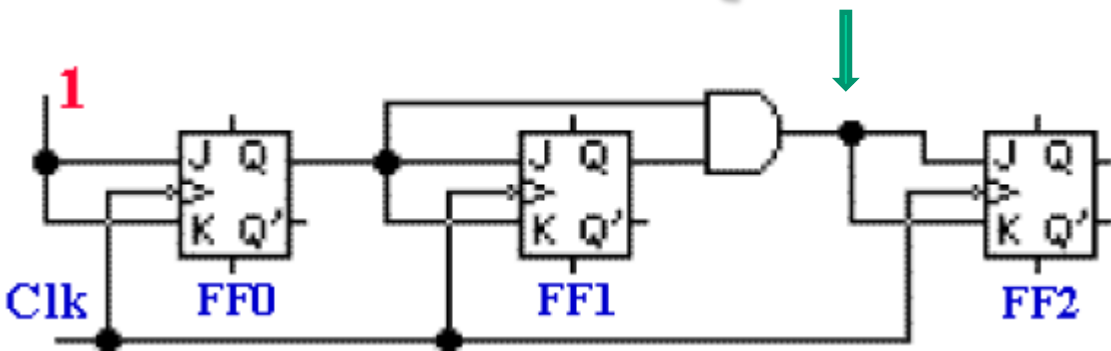From the K-maps we obtain after grouping: $\rightarrow \begin{cases} J0 = K0 = 1 \\ J1 = K1 = Q0 \\ J2 = K2 = Q1 * Q0 \end{cases}$



(b)

Output State Transitions			Flip-flop inputs					
Present State		Next State	J2 K2		J1 K1	J0 K0		
Q2	Q1	Q0	Q2	Q1	Q0			
0	0	0	0	X	X	1	X	
0	0	1	0	X	1	X	X	1
0	1	0	0	X	X	X	1	X
0	1	1	1	X	1	X	X	1
1	0	0	X	0	X	X	1	X
1	0	1	X	0	1	X	X	1
1	1	0	X	0	X	X	1	X
1	1	1	X	1	1	X	X	1

(0.5 points)


Q0 clock for Q1 (Q1 changes only when Q0 has negative drop → Extra do not cares X for J1 and K1 ⇒ **J1=K1=1**)

Output State Transitions			Flip-flop inputs					
Present State		Next State	J2 K2		J1 K1	J0 K0		
Q2	Q1	Q0	Q2	Q1	Q0			
0	0	0	X	0	X	1	X	
0	0	1	0	X	1	X	X	1
0	1	0	X	0	X	X	1	X
0	1	1	1	X	1	X	X	1
1	0	0	X	X	0	X	1	X
1	0	1	X	0	1	X	X	1
1	1	0	X	X	0	X	1	X
1	1	1	X	1	1	X	X	1

(0.5 points)

Q0 clock for Q2 → Extra do not cares X as indicated. If we derive the K-maps then we obtain **1 ⇒ J2=K2=Q1**


$$J0=K0=1, J1=K1=1, J2=K2=Q1$$

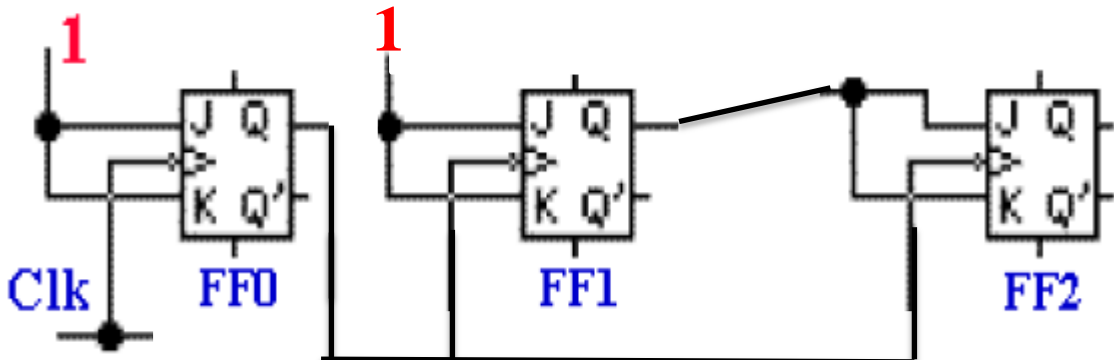

You can also consider Q1 clock for Q2 and then: **J1=K1=J2=K2=J0=K0=1** ¹⁴

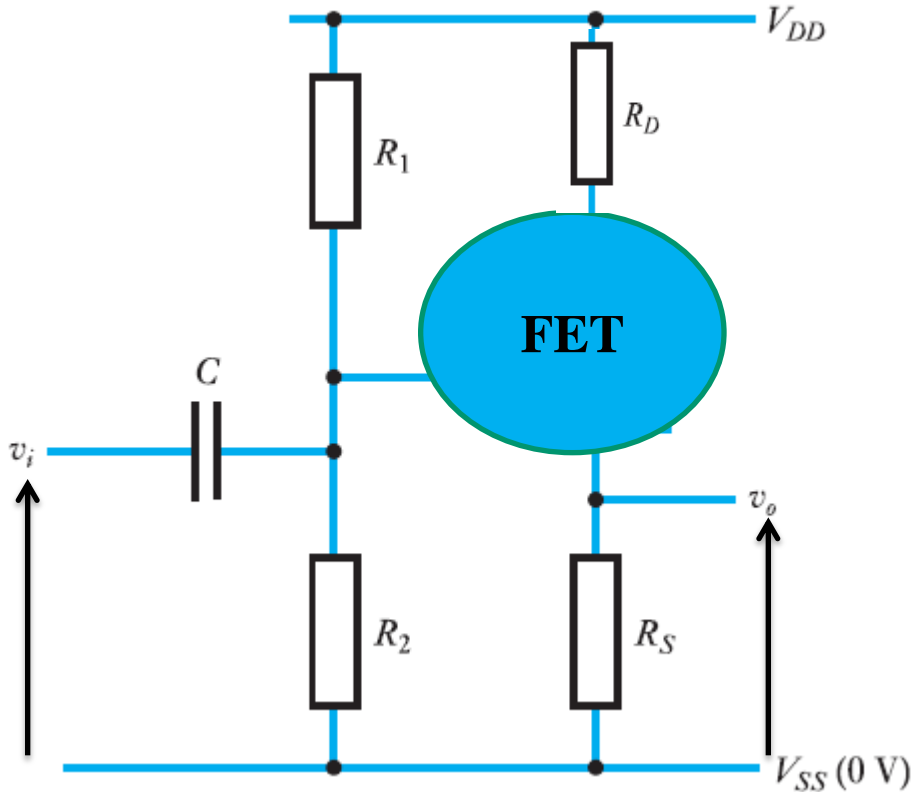Problem 6 (1.5 points)

Consider a FET amplifier as it is shown bellow:



Show that the amplification ratio of the input/output potential variations v_o/v_i is given by:

$$\frac{v_o}{v_i} = \frac{g_m R_s}{1 + g_m R_s + [(R_D + R_s) / r_d]}$$

with g_m the transconductance and r_d the differential resistance of the FET operating at saturation.

Solution Problem 6

First method: Solution for tough cookies!

I use differential analysis. [You can also use small signal circuit]

$$(1) V_o = I_D \cdot R_S, \quad \boxed{U_s \equiv V_o} \quad \boxed{U_g \equiv U_i}$$

$$(2) \tilde{V}_o = \tilde{I}_D R_S, \quad \tilde{I}_D = I_D + \underbrace{g_m U_{gs} + \frac{V_d - U_s}{r_d}}_{\text{change of FFT current because of } U_i}$$

$$U_s = \tilde{V}_o - V_o (\equiv U_o)$$

$$(2) - (1) \Rightarrow U_s = R_S \left[g_m U_{gs} + \frac{V_d - U_s}{r_d} \right] \quad (3)$$

$$(4) I_D = \frac{V_S}{R_S} = \frac{V_{DD} - V_D}{R_D}, \quad \tilde{I}_D = \frac{\tilde{V}_S}{R_S} = \frac{V_{DD} - \tilde{V}_D}{R_D} \quad (5)$$

$$(5) - (4) \Rightarrow \frac{U_s}{R_S} = - \frac{U_d}{R_D} \quad (6)$$

$$(6) \Rightarrow U_d = - \frac{R_D}{R_S} U_s \text{ and substitute in (3)}$$

$$U_s = g_m R_S (U_g - U_s) - R_S \frac{1 + \frac{R_D}{R_S}}{r_d} U_s$$

$$U_s = g_m R_S U_g - g_m R_S U_s - \frac{R_S + R_D}{r_d} U_s \Rightarrow$$


$$U_s \left[1 + g_m R_S + \frac{R_S + R_D}{r_d} \right] = g_m R_S U_g$$

$$U_s \equiv U_o, \quad U_i \equiv U_g$$

$$\frac{U_o}{U_i} = \frac{g_m R_S}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$$

Second method: Solution for normal cookies!

Small signal circuit

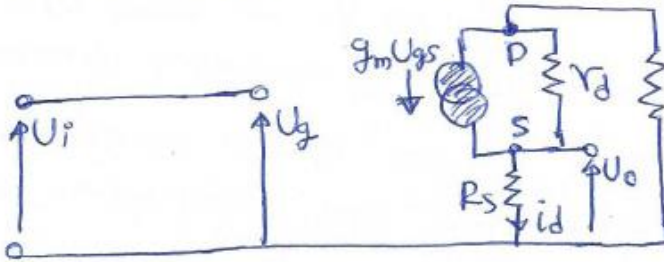

$$(1) U_o = U_s = i_d R_s, \quad i_b = g_m U_{gs} + \frac{U_d - U_s}{r_d} \quad (2)$$

$$i_b = -\frac{U_d}{R_D} = \frac{U_s}{R_s} \Rightarrow U_d = -\frac{R_D}{R_s} U_s \quad (3)$$

$$(1) + (2) + (3) = 0$$

$$U_s = R_s \left[g_m U_g - g_m U_s - \frac{1 + \frac{R_D}{R_s}}{r_d} U_s \right]$$

$$\Rightarrow U_s \left[1 + g_m R_s + \frac{R_D + R_s}{r_d} \right] = g_m R_s U_g$$

$$U_s \equiv U_o, \quad U_i = U_o$$

So we obtain

$$\boxed{\frac{U_o}{U_i} = \frac{g_m R_s}{1 + R_s g_m + \frac{R_D + R_s}{r_d}}}$$