

Mid-term Exam
Principles of Measurement Systems

(NAPMS05E.2010-2011)

Wednesday 06/10/2010 (09:00-11:00)

- Write your **name, student ID number and date of birth on the first page.**
- Write your **name on all pages and number the pages**
- This is **NOT an open book exam** - only a regular calculator is allowed.
- Pay attention to units. A numerical result without a unit will be considered wrong !
- You have **2 hours to complete the exam.**

Question 1

The table below characterizes a pressure gauge designed for operation at room temperature (25 °C, standard condition).

Pressure [bar]	1	2	3	4	5	6
I _{out} [mA] (25 °C)	4.0	7.2	10.4	13.6	16.8	20.0
I _{out} [mA] (35 °C)	3.5	7.2	10.9	14.6	18.3	22.0

We consider the "generalized model" : $O = a + K_I \cdot I_I + K_I \cdot I + K_M \cdot I_M \cdot I$

1.a. : To what "real-life" parameters correspond O, I, I_I and I_M in this particular case and what units do they have ? Motivate your answer based on the values in the above table.

1.b. : Determine values for a, K, K_I, K_M. Also note down the units of these parameters !

Question 2

A potentiometer ("potentiometric displacement sensor") has a total length of 10 cm and a resistance of 100 Ω.


2.a. : Calculate the supply voltage so that the power dissipation is 1 Watt

2.b. : Draw the Thévenin equivalent circuit for 7 cm displacement. Indicate the values for E_{Th}, Z_{Th} and include as well a load impedance.

2.c. : The potentiometer is connected to a recorder with a resistance R_L. Find R_L such that the recorder voltage is 5 % less than the open circuit voltage at 7 cm displacement.

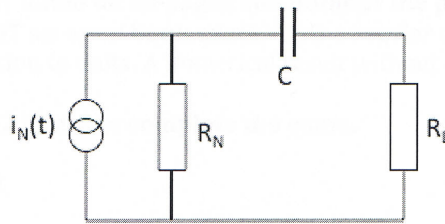Question 3

A current source $i(t)$ with an internal impedance of $100\text{ k}\Omega$ is capacitively coupled ($C = 1\text{ }\mu\text{F}$) to a recorder with impedance $100\text{ k}\Omega$. Both source and recorder are connected to the same ground potential. The corresponding circuit is shown in the figure below.



3.a. : Show that the transfer function $G(s)$ has the form : $G(s) = \frac{\Delta \bar{V}_L(s)}{\Delta \bar{i}_L(s)} = \frac{ks}{1 + \tau s}$

3.b. : Determine k and τ AND their units !

3.c. : What is the order of this system ?

3.d. : What is the amplitude ratio of an output sine wave when it's input to this system ?

3.e. : What is the asymptotic value of this amplitude ratio for very high frequency.

3.f. : For what value of ω is the amplitude ratio reduced to $1/\sqrt{2}$ of it's maximum value ? Make a comment about the bandwidth of this system.

3.g. : What is the phase of the output sine wave when it's input to this system ? Make a comment for very small and very large frequencies ($\omega \rightarrow 0$ and $\omega \rightarrow \infty$)

3.h. : Derive an expression for the step-function response of this system in the time domain ($V_L(t)$). Use for this the following Laplace transforms :

$1/s \rightarrow u(t) = \text{step function}$

$$\frac{1}{\alpha + s} \rightarrow e^{-t\alpha}$$