

1

Principles 6/10/2010

(a)

O = output current in mA

I = input pressure in bar

I_I = interfering input – degrees Celsius

I_M = modifying input – degrees Celsius

(b)

Standard condition :

$$O \text{ [mA]} = K \cdot I + a = 3.2 \text{ [mA/bar]} \times I \text{ [bar]} + 0.8 \text{ [mA]}$$

$$K = 3.2 \text{ [mA/bar]}$$

$$a = 0.8 \text{ [mA]}$$

(straight line between the 2 extreme points (1 bar, 4.0 mA) and (6 bar, 20 mA))

Non-standard conditions – since slope AND offset are changed the temperature difference of 10 °C can be considered both an interfering and modifying input.

$$O \text{ [mA]} = 3.7 \text{ [mA/bar]} \times I \text{ [bar]} - 0.2 \text{ [mA]}$$

$$3.7 \text{ [mA/bar]} = K + K_{M|I_M} \rightarrow K_{M|I_M} = K_M \cdot 10 \text{ }^\circ\text{C} = 0.5 \text{ [mA/bar]} \rightarrow K_M = 0.05 \text{ [mA/bar/}^\circ\text{C]}$$

$$-0.2 \text{ [mA]} = a + K_{I_I} \rightarrow K_{I_I} = K_I \cdot 10 \text{ }^\circ\text{C} = -1.0 \text{ [mA]} \rightarrow K_I = -0.1 \text{ [mA/}^\circ\text{C]}$$


2

(a)

$$P = \frac{V_s^2}{R} = 1 \text{ Watt}$$

$$V_s = 10 \text{ Volt}$$

(b)

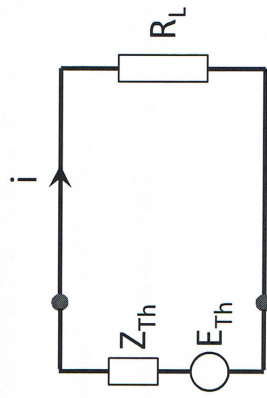

$$Z_{Th}^{-1} = (30 \Omega)^{-1} + (70 \Omega)^{-1}$$
$$Z_{Th} = 21 \Omega$$
$$E_{Th} = 7 \text{ V}$$


(c)

$$V_L = E_{Th} R_L / (Z_{Th} + R_L) = 0.95 E_{Th}$$

$$0.95 = R_L / (21 \Omega + R_L)$$

$$R_L = 399 \Omega$$

3

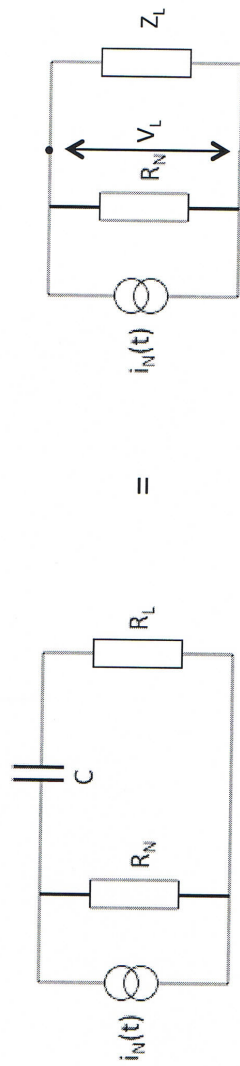

3.a) ANALYZE the electrical circuit, as was done for the NORTON equivalent circuit (p. 82-84)

First method : determine the voltage on the output terminals of the NORTON equivalent circuit

3

$$Z_L = \text{series impedances } R_L \text{ and } C, \text{ thus : } Z_L = R_L + Z_C = R_L + \frac{1}{sC}$$

$$Z_{TOT} = \text{Parallel impedances } R_N \text{ and } Z_L, \text{ thus : } \frac{1}{Z_{TOT}} = \frac{1}{R_N} + \frac{1}{Z_L} = \frac{1}{R_N} + \frac{1}{R_L + \frac{1}{sC}} = \frac{1}{R_N} + \frac{sC}{sCR_L + 1} = \frac{1 + sC(R_N + R_L)}{R_N(sCR_L + 1)}$$

$$Z_{TOT} = \frac{R_N(sCR_L + 1)}{1 + sC(R_N + R_L)}$$


$$V_L = i_N Z_{TOT} = i_N \frac{R_N(sCR_L + 1)}{1 + sC(R_N + R_L)}$$

$$\text{Voltage over the resistance } R_L = V_{R_L} = V_L \frac{R_L}{R_L + \frac{1}{sC}} = V_L \frac{sCR_L}{sCR_L + 1} = i_N \frac{sCR_L}{1 + sC(R_N + R_L)} = i_N \frac{R_N sCR_L}{1 + sC(R_N + R_L)}$$

In the spirit of the "impedance transfer function for the electrical circuit" (p. 86, Bentley), one recognizes easily

$$\text{the form of a transfer function } (V_{RL}/i_N) \frac{ks}{1 + \tau s}$$

3

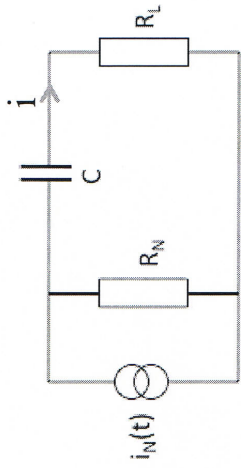

3.a) ANALYZE the electrical circuit, as was done for the NORTON equivalent circuit (p. 82-84)


Second method : use the current division rule in the NORTON circuit

$$i = i_N \frac{R_N}{R_N + R_L + \frac{1}{sC}}$$

$$V_{R_L} = iR_L = i_N \frac{R_L R_N}{R_N + R_L + \frac{1}{sC}} = i_N \frac{sCR_L R_N}{sC(R_N + R_L) + 1}$$

again one recognizes the form of $G(s) = \frac{ks}{1 + \tau s}$

3

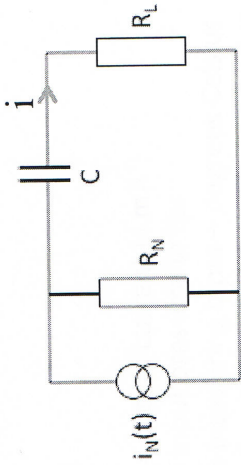

3.b) $k = CR_N R_L$

$\tau = C(R_N + R_L)$

$\tau = 0.2$ seconds

$k = 10^4$ seconds x Ohm

CT

3.c) 1st order

3.d) $G(s) = \frac{ks}{1 + \tau s}$

$$|G(s = j\omega)| = \left| \frac{jk\omega}{1 + j\tau\omega} \right| = \left| \frac{k\tau\omega^2 + jk\omega}{1 + (\tau\omega)^2} \right| =$$

$$\frac{\sqrt{(k\tau\omega^2)^2 + (k\omega)^2}}{1 + (\tau\omega)^2} = k\omega \frac{\sqrt{(\tau\omega)^2 + 1}}{1 + (\tau\omega)^2} = k\omega \frac{1}{\sqrt{1 + (\tau\omega)^2}}$$

amplitude of the input sine wave = 1
 amplitude of the output sine wave = 1. $|G(s=j\omega)|$
 ratio is thus just simply $|G(s=j\omega)|$

3.e) $\lim_{\omega \rightarrow \infty} |G(s = j\omega)| \approx \frac{k\omega}{\tau\omega} = \frac{k}{\tau}$

3.f) $|G(s = j\omega)| = k\omega \frac{1}{\sqrt{1 + (\tau\omega)^2}} = k\omega \frac{1}{\sqrt{1 + (\tau\omega)^2}} = \frac{1}{\sqrt{2}} \frac{k}{\tau}$

$\Rightarrow \omega^2 \frac{1}{1 + (\tau\omega)^2} = \frac{1}{2\tau^2}$

$\Rightarrow 2\tau^2\omega^2 = 1 + \tau^2\omega^2$

$\Rightarrow \omega = \frac{1}{\tau}$

bandwidth ranges from $1/\tau$ to infinity

3.g) phase = $\arg(G(j\omega)) = \tan^{-1}\left(\frac{1}{\omega\tau}\right)$

for ω very small the phase goes to 90 degrees
 for ω very big the phase goes to zero degrees.

3.h) output $f_0(s) = \frac{ks}{1 + \tau s} \cdot \frac{A}{s} = A \frac{k}{1 + \tau s}$

where A is the magnitude of the step function
 (Norton current $i_N = A$)

inverse Laplace transform :

$f_0(t) = i_N \frac{k}{\tau} \exp(-t/\tau) = i_N 50k\Omega \exp(-t/0.2 \text{ sec})$

CT