

Exam - PoMS, 20/02/2014

- Write each question on a sheet of paper.
- Write your **name** and **student ID** on each sheet.
- Pay attention to units. A numerical result without a unit will be considered wrong!
- Only a regular calculator is allowed.
- This is **NOT** an open book exam.
- You are allowed to bring one A4 page with your own notes (one side only).
- You have **3 hours** to complete the exam.
- Note: $\mathcal{L}(t^n e^{-at}) = \frac{n!}{(s+a)^{n+1}}$.

Question 1: General (2 points)

- a) What is the Nyquist sampling theorem and explain its underlying principle.
- b) What is reluctance and explain qualitatively the working principle of a variable reluctance tachogenerator.
- c) What is the working principle behind Amplitude Modulation (AM) and explain how such a technique can help to reduce external interferences?
- d) What is the working principle behind Frequency Modulation (FM) and explain how such a technique can help to reduce external interferences?

Question 2: A force measurement system (2 points)

A force measurement system consists of linear elements and has an overall steady-state sensitivity of unity. The dynamics of the system are determined by the second-order transfer function of the sensing element, which has a natural frequency $\omega_n = 35$ rad/s and a damping ratio $\xi = 0.15$. Calculate the system dynamic error corresponding to the periodic input force signal:

$$F(t) = 50 (\sin 10t + 1/3 \sin 30t + 1/5 \sin 50t),$$

with t in seconds and $F(t)$ in Newtons.

Question 3: A strain gauge measurement system (2 points)

Consider a strain gauge measurement system as indicated in Fig. 1. The sensor consists of 4 strain gauges for which R_1 and R_4 are placed in tensile mode, e.g. $R_1 = R_4 = R_0(1 + Ge)$, and R_2 and R_3 in compressive mode, e.g. $R_2 = R_3 = R_0(1 - Ge)$, with $R_0 = 100 \Omega$ at a temperature of $T = 20 \text{ }^\circ\text{C}$ and a gauge factor of $G = 2$. The power supply has a voltage of $V_S = 12 \text{ V}$. The sensor is connected to a recorder element via a cable with a total resistance of $R_C = 50 \Omega$. The recorder has a loading resistance of $R_L = 10 \text{ k}\Omega$.

- a) Find the Thévenin equivalent voltage, V_{Th} , and the corresponding impedance, Z_{Th} , of the sensor element.
- b) Calculate the voltage over R_L , V_L , for a strain of $e = 10^{-3}$ at $T = 20 \text{ }^\circ\text{C}$. How large is the loading effect on the recorder?
- c) The temperature of the sensor increases, which leads to an increase in the resistances of the strain elements, R_1 , R_2 , R_3 , and R_4 , by 5Ω . What is the main underlying physical mechanism that increases the resistance of a conductor due to an increase in temperature? Discuss the influence of this effect on V_L .
- d) The output voltage on the recorder, V_L , is considered to be too small. Redesign the measurement system in such a way that V_L is amplified by a factor 10. For this, introduce an ideal operational amplification element without changing the sensor and recorder elements and their parameters.

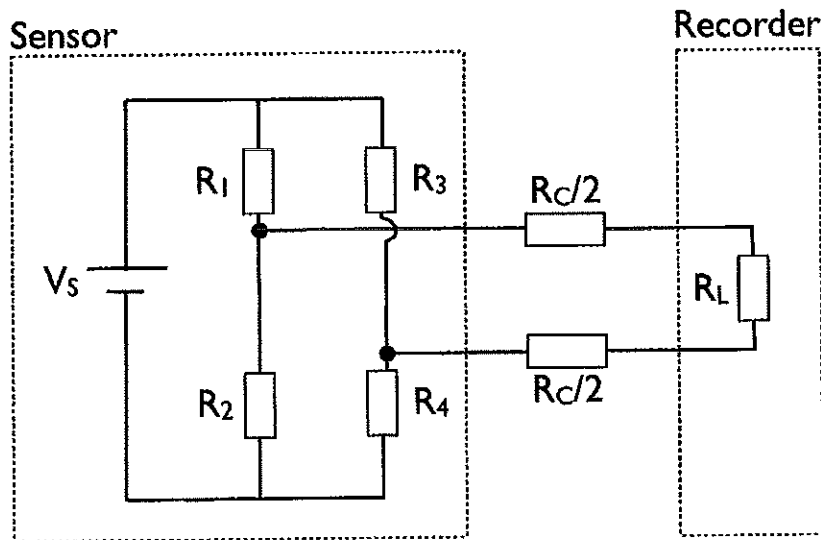


Figure 1: Figure corresponding to question 3.

Question 5: A current transmitter (2 points + 1 bonus point)

Consider a current transmitting system as indicated in Fig. 3. A sensor consists of a Norton current source connected to a resistance $R_N=1\text{ M}\Omega$ and a capacitor $C_N=1000\text{ pF}$. The indicator reads the voltage (V_L) over a resistance $R_L=10\text{ k}\Omega$. An interfering series mode voltage V_{SM} can be present on the system.

- a) Take $V_{SM}=0$. Show that the transfer function is given by

$$\frac{\Delta \tilde{V}_L}{\Delta \tilde{i}_N}(s) = R' \left(\frac{1}{1 + s\tau} \right), \quad (1)$$

with $R' = R_N R_L / (R_N + R_L) = 9.9\text{ k}\Omega$ and $\tau = C_N R' = 9.9\text{ }\mu\text{s}$.

- b) The current i_N increases suddenly (as a step function) to 1 mA at $t=0$ from a steady-state condition with $i_N = V_L = 0$ at a time $t < 0$. Give an expression for $V_L(t)$ and make a sketch of its time dependence.
- c) Consider a steady-state situation with an interfering voltage $V_{SM}=10\text{ V}$ together with $i_N=1\text{ mA}$. How large is the influence of the interfering voltage on V_L ? Give the signal-to-noise ratio (S/N) in dB.

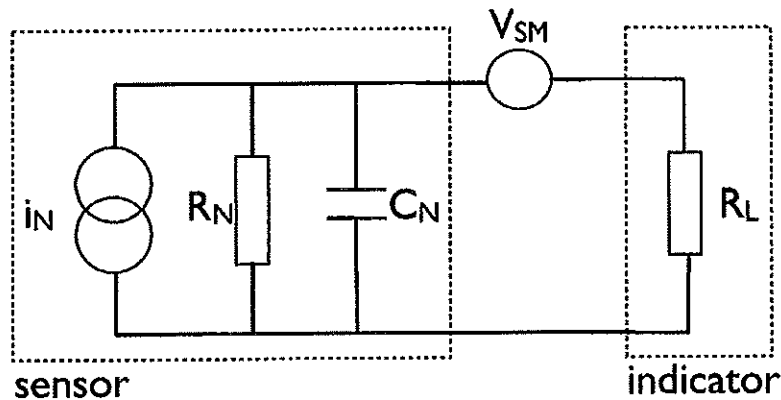


Figure 3: A current transmitter.

Question 4: A potentiometric displacement sensor (2 points)

A potentiometer has a total length of d_T and a resistance of R_P . The supply voltage of the potentiometer is indicated as V_S . The potentiometer is connected to a recorder with a resistance R_L . The setup is illustrated in Fig. 2.

- a) Show that the voltage at the recorder, V_L , is given by

$$V_L = V_S \frac{x}{(R_P/R_L)x(1-x) + 1},$$

with $x = d/d_T$ and d is the displacement. [Hint: you can make use of the Thévenin equivalent circuit law.]

- b) In the ideal case, $R_L \gg R_P$, we would have the relation $V_L/V_S \approx x$. Estimate the maximum non-linearity of V_L/V_S for $R_L=1 \text{ k}\Omega$ and $R_P=100 \text{ }\Omega$. At which value of x does one find the maximum non-linearity?

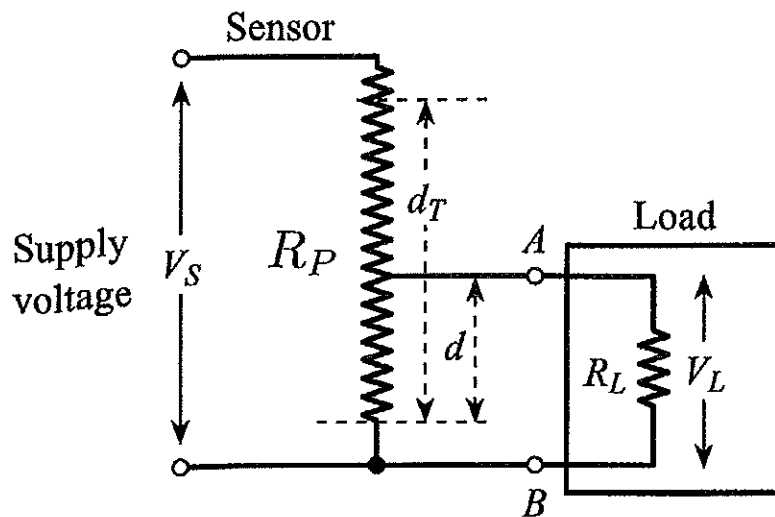


Figure 2: A potentiometric displacement sensor.

Steady-state sensitivity of 1 : $\frac{1}{k} = 1 \left(\frac{m}{N}\right)$

natural frequency

$$: \omega_n = \frac{35}{35} \left(\frac{\text{rad}}{s}\right)$$

damping ratio

$$: \zeta = 0.15$$

2

$$E(t) = F_{out}(t) - F_{in}(t)$$

From page 63 of Bentley : $F_{out}^{(h)}(t) = \hat{I}^{(h)}(k) \cdot |G(j\omega_n)| \cdot \sin(\omega_n t + \phi_n)$

$$\Rightarrow F_{out}(t) = 50 \left[|G(10j)| \sin(10t + \phi_{10}) + \frac{|G(30j)|}{3} \sin(30t + \phi_{30}) + \frac{|G(50j)|}{5} \sin(50t + \phi_{50}) \right]$$

Second-order transfer function :

$$\begin{cases} G(s) = \frac{1}{\frac{1}{\omega_n^2} s^2 + \frac{2\zeta}{\omega_n} s + 1} \\ |G(j\omega)| = \frac{1}{\sqrt{\left(1 - \frac{\omega^2}{\omega_n^2}\right)^2 + 4\zeta^2 \left(\frac{\omega}{\omega_n}\right)^2}} \end{cases}$$

$$\Rightarrow |G_{10}(j)| = \frac{1}{\sqrt{\left(1 - \frac{10^2}{35^2}\right)^2 + 4 \times 0.15^2 \times \left(\frac{10}{35}\right)^2}} = 1.08$$

$$\& \phi_{10} = \arg G(j\omega) \Big|_{\omega=10 \left(\frac{\text{rad}}{s}\right)} = -\arctan \left[\frac{2\zeta \frac{\omega}{\omega_n}}{1 - \frac{\omega^2}{\omega_n^2}} \right]_{\omega=10 \left(\frac{\text{rad}}{s}\right)} = -5.33^\circ - 0.093$$

Finally, we will have : $|G(30j)| = 2.71$, $|G(50j)| = 0.89$

, $\phi_{30} = -44.0^\circ$, $\phi_{50} = -157.6^\circ$

Thus,

$$-0.77$$

$$+0.39$$


$$E(t) = 50 \left[1.08 \sin(10t - 5^\circ) - \sin(10t) \right] + \frac{50}{3} \left[2.71 \sin(30t - 44^\circ) - \sin(30t) \right] + \frac{50}{5} \left[0.89 \sin(50t - 158^\circ) - \sin(50t) \right]$$

1/2

5

a)

sensor =
(Wheatstone bridge)

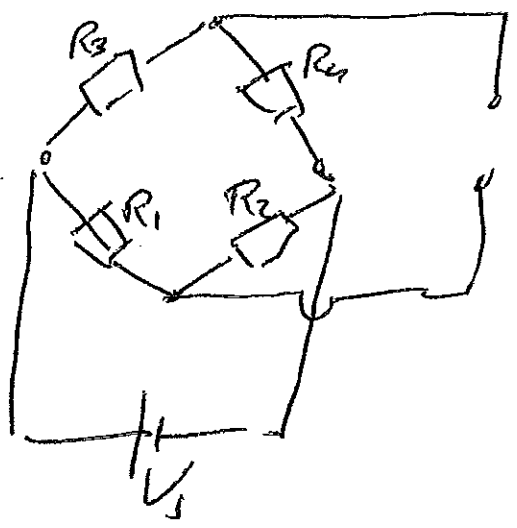


$$E_{th} = \left[\frac{R_1 R_4 - R_2 R_3}{(R_1 + R_2)(R_3 + R_4)} \right] = V_s \left[\frac{R_0^2 (1+ge)^2 - R_0^2 (1-ge)^2}{4R_0^2} \right]$$

$$= V_s \left[\frac{4ge}{4} \right] = \underline{\underline{V_s ge}}$$

$$Z_{th} = \frac{R_3 R_4}{R_3 + R_4} + \frac{R_1 R_2}{R_1 + R_2} = \frac{R_0^2 (1-ge)(1+ge)}{2R_0} + \frac{R_0^2 (1+ge)(1-ge)}{2R_0}$$


$$= R_0 (1-ge)(1+ge) = \underline{\underline{R_0 [1-(ge)^2]}}$$
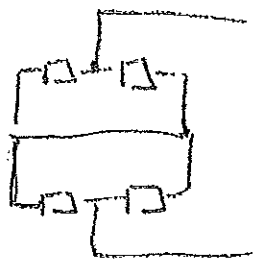
$$\frac{R_2}{R_2 + R_1} - \frac{R_4}{R_3 + R_4} = \frac{R_2(R_3 + R_4) - R_4(R_2 + R_1)}{(R_2 + R_1)(R_3 + R_4) - R_3 R_4 - R_1 R_4}$$



(1/2)
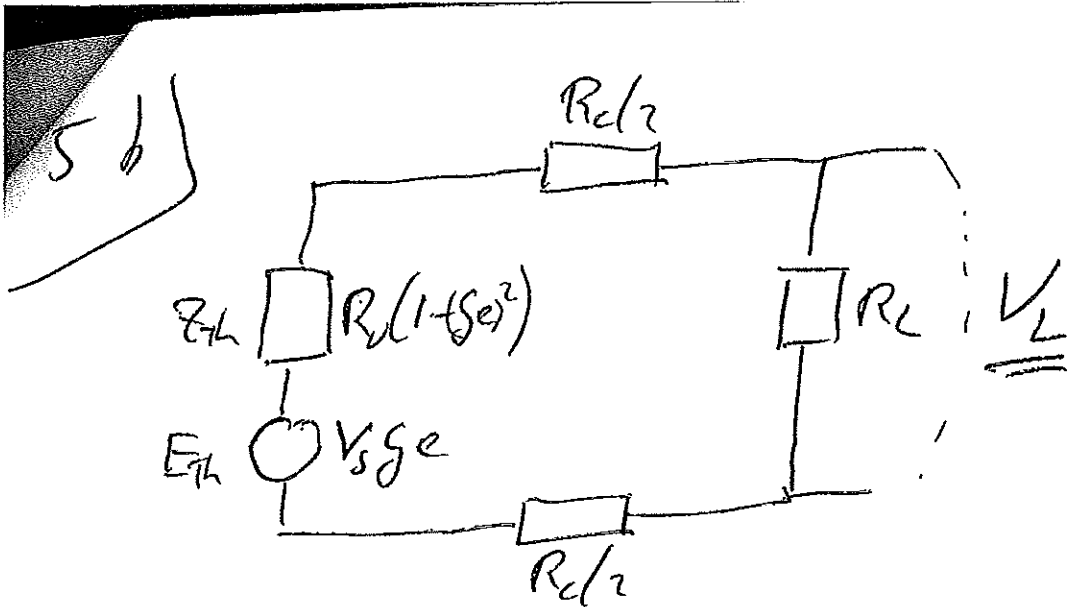
$$V_{E_{th}} = \frac{R_1}{R_2 + R_1} - \frac{R_3}{R_3 + R_4}$$



$$V_L = E_{Th} \frac{R_L}{R_L + R_c + Z_{Th}} = V_s g_e \frac{10 \cdot 10^3 \Omega}{10 \cdot 10^3 + 50 + 100 \Omega}$$

$$= V_s \cdot g_e \cdot 0,985 = \underline{\underline{23.6 \text{ mV}}}$$

$$\underline{\text{loading effect}} : 1 - 0,985 = \underline{\underline{0.015}} = \underline{\underline{1.5\%}}$$

(1/2)

5c) temp. increase of conductor \Rightarrow τ reduces \Rightarrow $R \uparrow$
 (time between interactions smaller)

$$R = \rho \frac{l}{A} = \frac{m_e}{e^2 n \tau} \frac{l}{A}$$

temperature effect \Rightarrow $R_1 = R_2 = R_3 = R_4 = R_0 (1 + \alpha \Delta T)$
 only


$$E_{Th} \text{ from } \Delta T \Rightarrow E_{Th} = \frac{R_1 R_4 - R_2 R_3}{(R_1 + R_2)(R_3 + R_4)} = 0$$

$$Z_{Th} \text{ from } \Delta T \Rightarrow Z_{Th} = \frac{R_3 R_4}{R_3 + R_4} + \frac{R_1 R_2}{R_1 + R_2}$$

$$= R_0 (1 + \alpha \Delta T) = 105 \Omega$$


\Rightarrow hardly changes V_C !
(1)

5 d

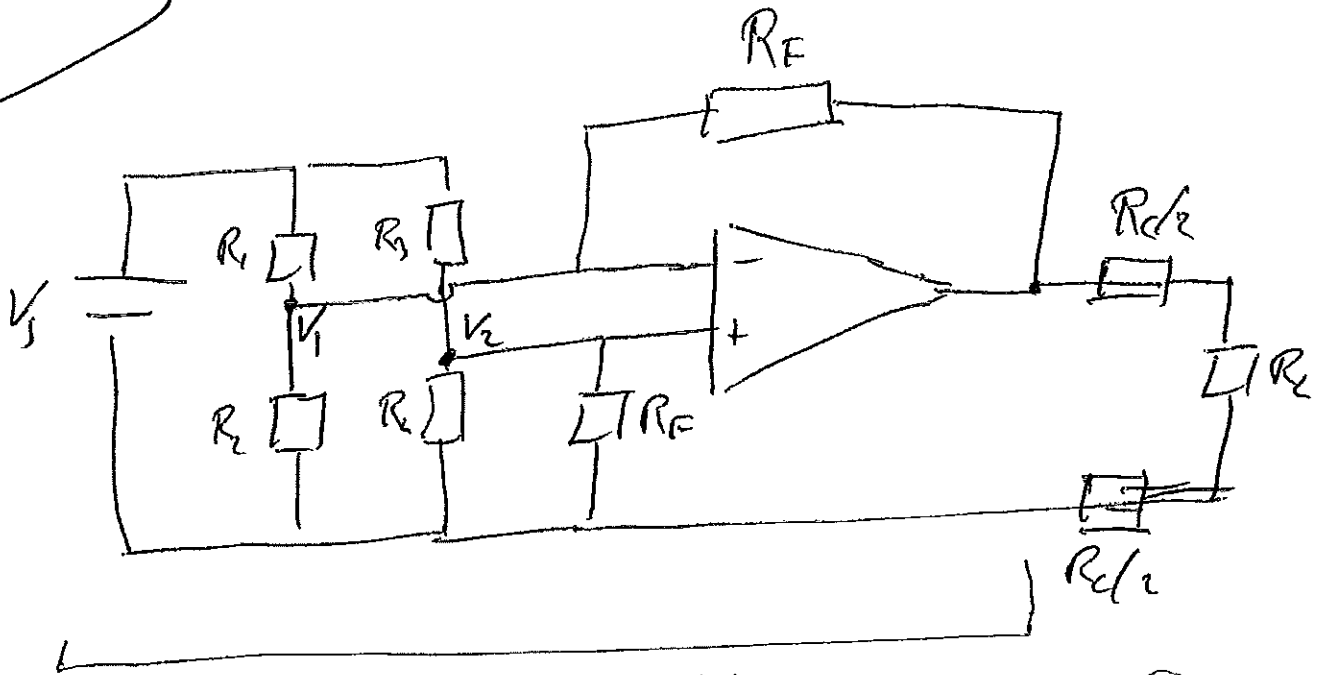

Equivalent to diff. amplifier

(1)

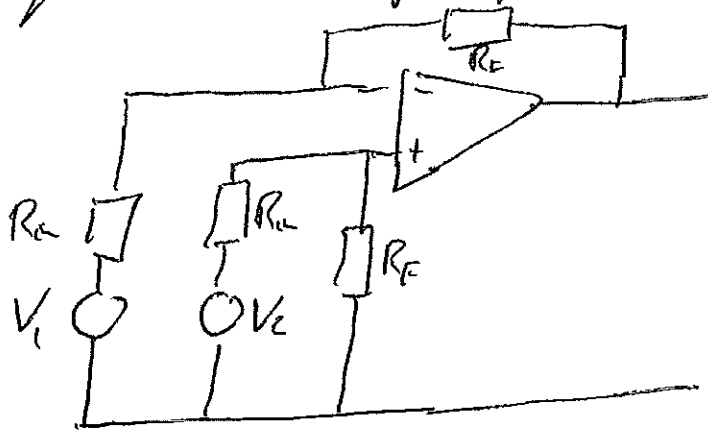

$$V_{out} = (V_2 - V_1) \frac{R_F}{R_{in}}$$

$$R_{in} = \frac{R_1 R_2}{R_1 + R_2} \approx \frac{R_0}{2} \quad [(\beta e)^1 \text{ small!}]$$

$$V_1 = V_s \frac{R_2}{R_1 + R_2} = V_s \frac{R_0(1 - \beta e)}{2R_0} = \frac{V_s}{2} (1 - \beta e)$$

$$V_2 = V_s \frac{R_4}{R_3 + R_4} = \frac{V_s}{2} (1 + \beta e)$$

Cont'd


$$\Rightarrow V_{out} = \frac{2R_F}{R_0} V_s g_e$$

factor 10 Amplification, $\Rightarrow \frac{2R_F}{R_0} = 10$

$$\hookrightarrow R_F = 5R_0 = 500 \Omega$$

Question 4)

equivalent circuit :

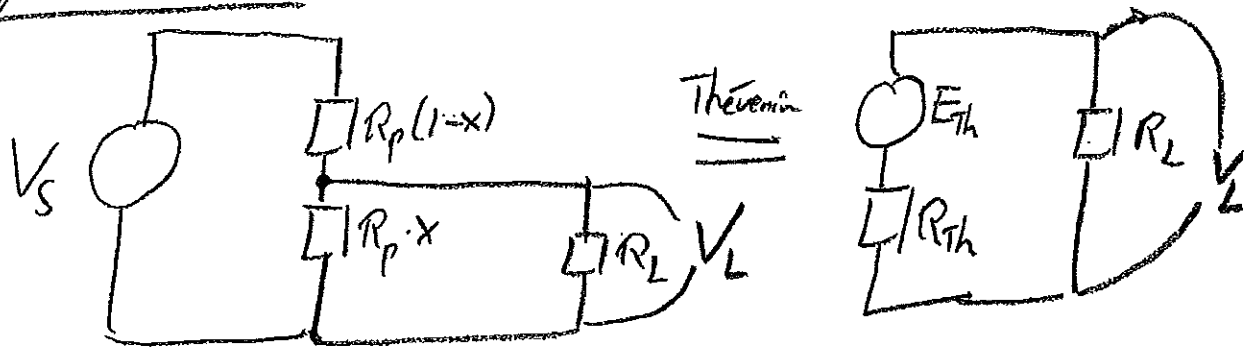


a)

E_{Th} : open circuit ($R_L \rightarrow \infty$)

$$E_{Th} = V_s \frac{R_p \cdot x}{R_p \cdot x + R_p(1-x)} = \underline{\underline{V_s \cdot x}}$$

R_{Th} : short cut V_s :

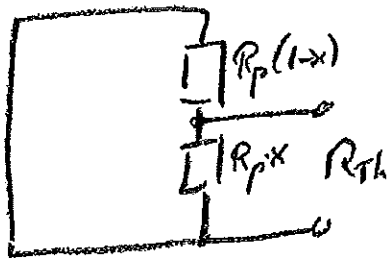

$$\Rightarrow R_{Th} = R_p(1-x) \parallel R_p \cdot x$$

$$\Rightarrow \frac{1}{R_{Th}} = \frac{1}{R_p(1-x)} + \frac{1}{R_p \cdot x}$$


$$\Rightarrow R_{Th}^{-1} = \frac{R_p \cdot x + R_p(1-x)}{R_p^2(1-x)x} \Rightarrow \underline{\underline{R_{Th} = R_p \cdot x(1-x)}}$$

Hence,

$$V_L = E_{Th} \frac{R_L}{R_L + R_{Th}} = V_s \cdot x \cdot \frac{R_L}{R_L + R_p \cdot x(1-x)} = \underline{\underline{V_s \frac{x}{(\frac{R_p}{R_L})x(1-x) + 1}}}$$

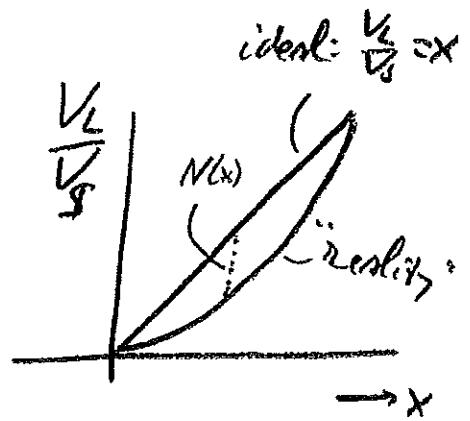Question 4, cont'd

$$b) \frac{V_L}{V_S} = \frac{x}{\left(\frac{R_p}{R_L}\right)x(1-x) + 1} \Rightarrow$$



non-linearity of V_L/V_S :

$$\begin{aligned} N(x) &= x - \frac{V_L}{V_S} = x \left[1 - \frac{1}{0.1x(1-x) + 1} \right] \\ &= x \left[\frac{0.1x(1-x) + 1}{0.1x(1-x) + 1} - \frac{1}{0.1x(1-x) + 1} \right] = x \frac{0.1x(1-x)}{0.1x(1-x) + 1} \\ &= 0.1x^2(1-x) = 0.1[x^2 - x^3] \end{aligned}$$


maximum non-linearity

$$\frac{dN}{dx} = 0.1[2x - 3x^2] = 0 \Rightarrow x = \frac{2}{3}$$

$$\begin{aligned} N_{\max} &= N\left(x = \frac{2}{3}\right) = 0.1 \left[\frac{4}{9} - \frac{8}{27} \right] = 0.1 \frac{4}{27} = \frac{4}{270} \\ &= \underline{\underline{1.48\%}} \end{aligned}$$

(45)


Current Transmitter

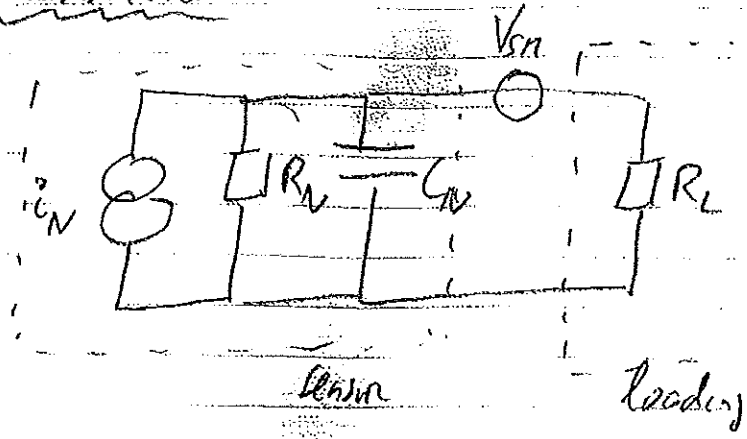


- $R_L = 10 \text{ k}\Omega$
- $R_N = 1 \text{ k}\Omega$
- $C_N = 1000 \text{ pF}$

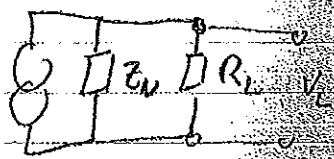(a) $\frac{\Delta V_L}{\Delta i_N}(s)$ with $V_N = 0$

$$Z_N = R_N // C_N = \frac{R_N \cdot \frac{1}{sC_N}}{R_N + \frac{1}{sC_N}} = \frac{R_N}{sC_N R_N + 1}$$


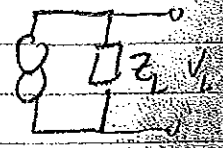
$$Z_L = R_L // Z_N = \frac{Z_N R_L}{Z_N + R_L} = \frac{\frac{R_N R_L}{sC_N R_N + 1}}{\frac{R_N}{sC_N R_N + 1} + R_L} = \frac{R_N R_L}{R_N + R_L + sC_N R_N R_L}$$




$$= \frac{R_N R_L}{R_N + R_L} \left[\frac{1}{1 + sC_N \left(\frac{R_N R_L}{R_N + R_L} \right)} \right] = R' \left(\frac{1}{1 + s\tau} \right) = G(s)$$

$R' \approx R_L = 10 \text{ k}\Omega (= 9.9 \text{ k}\Omega)$

$\tau = C_N R' \approx 10^{-5} \text{ s} = 10 \mu\text{s} (= 9.9 \mu\text{s})$

with $\tau = C_N R'$
 $R' = \frac{R_N R_L}{R_N + R_L}$

(b.)

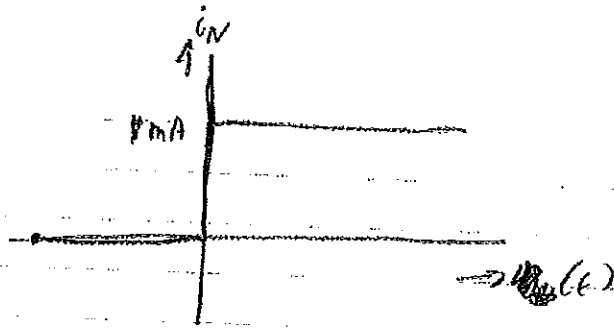

$$i_N(t) = \mu(t) \cdot 1 \text{ mA}$$

$$\Delta i_N(s) = \frac{1}{s} \cdot 1 \text{ mA}$$

$$\Delta V_L = \Delta i_N \cdot \frac{R}{1+\tau s}$$

$$= \frac{1}{s} \cdot \frac{1}{1+\tau s} \cdot 9.9 \text{ V}$$

$$= \frac{A}{s} + \frac{B}{1+\tau s}$$

$$\Rightarrow A(1+\tau s) + Bs = 1$$

$$A + (A\tau + B)s = 0$$

(for all s)


$$= \frac{1}{s} - \frac{\tau}{1+\tau s}$$

$$\Rightarrow A=1 \text{ and } A\tau + B = 0$$

$$\Rightarrow B = -A\tau = -\tau$$

$$= \frac{1}{s} - \frac{1}{\frac{1}{\tau} + s}$$
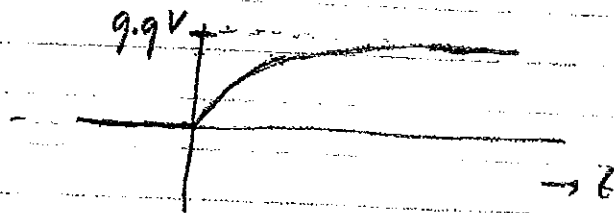
$$\xrightarrow{f^{-1}} V_L(t) = 9.9 \mu(t) [1 - e^{-t/\tau}] \text{ [V]}$$



(c) bandwidth $0 \leftrightarrow \frac{1}{\tau} = 10^5 \frac{\text{rad}}{\text{s}} = \frac{10^5}{2\pi} \text{ Hz}$


\Downarrow
 ω_b

\Downarrow
 $f_b = \frac{\omega_b}{2\pi}$

c)

~~10V~~ $V_{SM} = 10V$

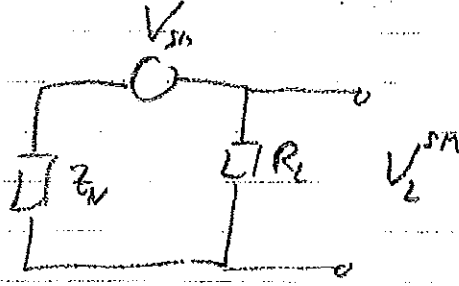distorsion en V_L : V_L^{SM}
(superposition)



$$V_L^{SM} = V_{SM} \cdot \frac{R_L}{R_L + R_N} \xrightarrow{\text{steady state}} V_{SM} \cdot \frac{R_L}{R_L + R_N} = \frac{V_{SM}}{101} = \underline{\underline{0.1V}}$$

$$V_L = 9.9 + 0.1 V = \underline{\underline{10V}}$$

superposition

$$\frac{S}{N} = 20 \log_{10} \left(\frac{10V}{0.1V} \right) = \underline{\underline{40 dB}}$$