YOUR NAME:	ID:_s	DOB:	/_	/19_	_

Department/Program: TN / N / TBK / BMT / ...

## Final Exam

# Principles of Measurement Systems (NAPMS.2008-2009.1a)

Friday, February 6, 2009 (14:00-17:00)

Please write your name, student ID number and date of birth on this or the first page, only your name on <u>all</u> subsequent pages, and number the pages. Don't forget to hand in all relevant paperwork.

This is <u>not</u> an open-book exam, so please remove all other documents.

Read carefully. Pay attention to units. A numerical result without, or with wrong units, will be considered incorrect. You may assume that I know the answer to the questions posed; Therefore, give derivations and/or motivate your answers as appropriate! If you cannot answer the first part of a question, make a (educated) guess, and continue with the rest... Success!

You may use the following table:

time-domain $f(t)$	s-domain $\tilde{f}(s)$
$\delta(t)$	1
1	$\frac{1}{s}$
t	$\frac{s}{s^2}$
$e^{at}$	$\frac{1}{s-a}$
$1-e^{-at}$	$\frac{a}{s(s+a)}$
$\sin(\omega t)$	$\frac{\omega}{s^2 + \omega^2}$
$\cos(\omega t)$	$\frac{s}{s^2 + \omega^2}$
$e^{at}g(t)$	$\tilde{g}(s-a)$
g(at)	$\frac{1}{a}\tilde{g}\left(\frac{s}{a}\right)$
f(t)	$\int_{0^{-}}^{\infty} f(t)e^{-st}dt \qquad \qquad *)$
f'(t)	$s \cdot \tilde{f}(s) - f(0^{-})$

<sup>\*)</sup> Note: The lower bound of the integral being equal to 0 signifies that the origin is fully included in the evaluation of the integral.

### Question 1 (Chapter 3)

A simple temperature measurement system consists of a specialized temperature sensor (the AD592 from Analog Devices) operating from a power supply voltage of 12V and generating a current proportional to the temperature in degrees Kelvin. The current is converted to a voltage reading by a resistor and buffer amplifier combination. The output is interpreted by a microcomputer with display. The system is represented in Figure 2, and characterized by the following steady-state parameters for an input temperature T of 30 °C:

$$Ms = 10^{-4} \,\mu\text{A/K}^{2} \qquad \qquad \sigma_{Ms} = 0 \,\mu\text{A/K}^{2} \\ K_{s} = 1 \,\mu\text{A/K} \qquad \qquad \sigma_{Ks} = 0 \,\mu\text{A/K} \\ H_{s} = 0.1 \,\mu\text{A} \qquad \qquad \sigma_{Hs} = 10^{-3} \,\mu\text{A} \\ M_{a} = 10^{4} \,\Omega \qquad \qquad \sigma_{Ma} = 30 \,\Omega \\ K_{a} = -150 \,\text{mV/mA}^{0.5} \qquad \qquad \sigma_{Ka} = 0 \,\text{mV/mA}^{0.5} \\ H_{a} = -3 \,\text{mV} \qquad \qquad \sigma_{Ha} = 0 \,\text{mV} \\ K_{d} = 100 \,\text{K/V} \qquad \qquad \sigma_{Kd} = 0 \,\text{K/V} \\ H_{d} = -0.5 \,\text{K} \qquad \qquad \sigma_{Hd} = 0 \,\text{K} \\ \end{cases}$$

The sub-systems are described by the following equations:  $i = H_s + K_s \cdot T + M_s \cdot T^2$ ,  $V = H_a + K_a \cdot i^{0.5} + M_a \cdot i$ , and  $T_M = H_d + K_d \cdot V$ .



Figure 1. Block diagram of the temperature measurement system

- a) Calculate the mean of the output reading  $T_M$  when the input temperature is T = 30 °C.
- b) Calculate the standard deviation of the output reading  $T_M$  when the input temperature is T = 30 °C.
- c) Determine the <u>accuracy</u> and the <u>precision</u> of the measurement at 30 °C in terms of the results of a) and b).
- d) Identify the one parameter of the above system that dominates the uncertainty in the temperature reading.

Question 2 (Chapter 6)

A pressure sensor with built-in current transmitter (characterized by its Norton equivalent circuit: current source  $i_N$  with shunt resistance  $R_N$ ) is read out by a recorder with load resistance  $R_L$ . The capacitive coupling to a nearby power cable and earth plane (same as the recorder ground) can be described by the parasitic capacitors  $C_1$ ,  $C_2$ ,  $C_3$ , and  $C_4$ , as shown in Figure 2.

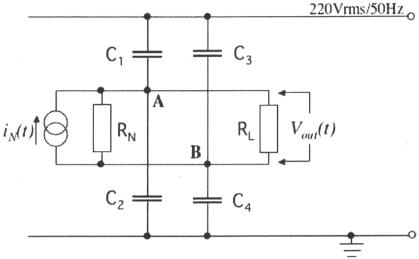


Figure 2. Equivalent circuit of pressure transducer and recorder, showing capacitive coupling to power cable and earth plane.  $R_N=100 \text{ k}\Omega$ ,  $R_L=1 \text{ k}\Omega$ ,  $C_1=50 \text{ pF}$ ,  $C_2=55 \text{ pF}$ ,  $C_3=80 \text{ pF}$ ,  $C_4=85 \text{ pF}$ 

Assume for the moment that  $i_N = 0$  A and  $R_N = R_L = \infty \Omega$ .

- a. Derive an expression for the common mode voltage (rms) seen by the recorder, and evaluate it numerically.
- b. Derive an expression for the series mode voltage (rms) seen by the recorder, and evaluate it numerically.

The current is given by  $i_N(t) = c \cdot \sin(\omega t)$ , with c = 6.3 mA and  $\omega = 1$  kHz.

- c. Ignoring the influence of the capacitive coupling, calculate the <u>rms</u> signal registered by the recorder.
- d. Discuss strategies for reduction of the capacitive coupling (considering the physical characteristics that are at the origin of the capacitive coupling).
- e. Estimate the signal-to noise ratio of the measurement, provided that the recorder has a CMRR=60 dB and that the sole source of noise is the capacitive coupling to the power cable.

### Question 3 (Chapter 4)

A second-order system with transfer function G(s) is subjected to a unit step function (i.e., the Heaviside function  $H_0(t)$ ) at the input x.

$$G(s) = \frac{2}{s^2 + 2s + 2}$$

- a) Give the expression for  $\Delta \tilde{y}(s) = G(s) \cdot \Delta \tilde{x}(s)$ .
- b) Apply the final value theorem to calculate the steady-state value of the output (numerical result only is insufficient!).
- c) Expand  $\Delta \tilde{y}(s) = G(s) \cdot \Delta \tilde{x}(s)$  in relevant partial fractions.
- d) Derive the unit step time response function  $\Delta y(t)$  for this system.
- e) Sketch  $\Delta y(t)$ .

#### Question 4 (Chapter 8)

Figure 1 gives the schematic diagram of a thermocouple temperature sensor. The thermocouple is made up of Ni-Cr lead wires, a copper thermocouple wire (A, with Seebeck coefficient  $S_A$ ), and a constantan thermocouple wire (B, with Seebeck coefficient  $S_B$ ). The reference junction is kept in a bath of melting ice. Table I lists the Seebeck coefficients of a number of common materials.

- a) Derive an integral expression for the voltage  $V_{out}$  at the measurement terminals.
- b) What is the predicted output voltage at a tip temperature of 100 °C (measured with an ideal voltmeter)?.
- c) The length of the thermocouple wires A and B is increased from 5 to 50 cm. The accuracy of the measurement improves. Give a plausible explanation.

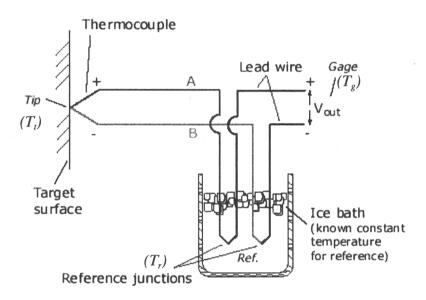


Figure 1. Thermocouple arrangement.

Table I. Seebeck coefficients of various metals at 0 °C.

Material	Seebeck Coeff. [µV/°C]	Materia	Seebeck Coeff. [µV/°C]	Material	Seebeck Coeff. [µV/°C]
Aluminum	3.5	Gold	6.5	Rhodium	6.0
Antimony	47	Iron	19	Selenium	900
Bismuth	-72	Lead	4.0	Silicon	440
Cadmium	7.5	Mercur	y 0.60	Silver	6.5
Carbon	3.0	Nichro	me 25	Sodium	-2.0
Constantan	-35.1	Nickel	-15	Tantalum	4.5
Copper	7.6	Platinu	m 0	Tellurium	500
Germanium	300	Potass	ium -9.0	Tungsten	7.5

... End of the Exam.